


Voltage Source 1

v_{s1}

$R_{Th} = R_{Th<}$




Resistor: variable 5

(CdS Photocell)

R_{CdS}


$R_{Th} = R_{CdS} + R_{Th<}$



Voltage Source 2

v_{s2}


$R_{Th} = R_{Th<}$



V-Divider 6

$G = \frac{R_2}{R_1 + R_2 + R_{Th<}}$


$R_{Th} = (R_1 + R_{Th<}) \parallel R_2$



Resistor 3

R

$R_{Th} = R + R_{Th<}$



Potentiometer 7


$G_1 = \frac{R_b + R_{Th2<}}{R_{pot} + R_{Th<Tot}}$

$G_2 = \frac{R_a + R_{Th1<}}{R_{pot} + R_{Th<Tot}}$

$R_{pot} = R_a + R_b$

$R_{Th<Tot} = R_{Th1<} + R_{Th2<}$

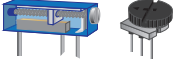$R_{Th} = (R_a + R_{Th1<}) \parallel (R_b + R_{Th2<})$




Resistor: variable 4

(Thermistor)

R_T

$R_{Th} = R_T + R_{Th<}$



Resistor: parallel 8

$G = \frac{R_p}{R_p + R_{Th<}}$

$R_{Th} = R_p \parallel R_{Th<}$

