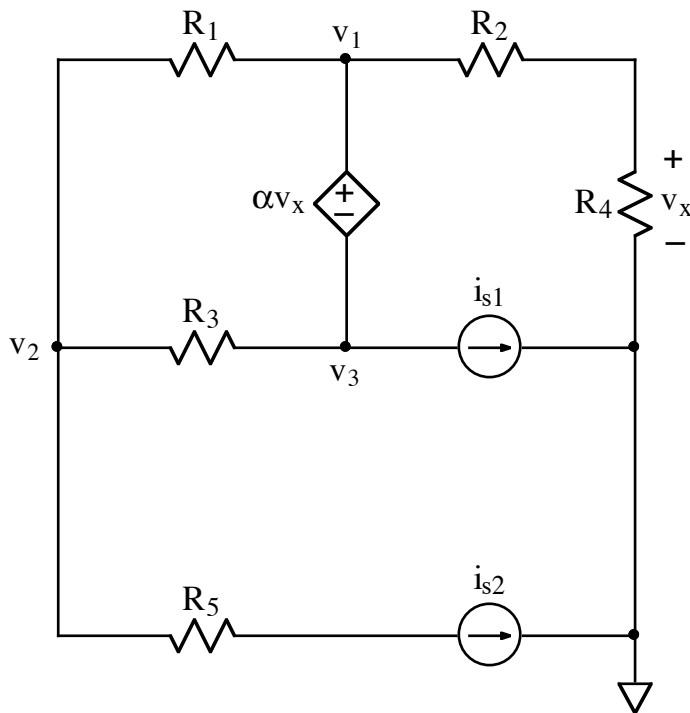


Ex:



$$v_1 \left(\frac{1}{R_1} + \frac{1}{R_2 + R_4} \right) - v_2 \left(\frac{1}{R_3} + \frac{1}{R_1} \right) + v_3 \frac{1}{R_3} + i_{s1} = 0 \text{ A}$$

$$v_1 - v_3 = \alpha v_1 \left(\frac{R_4}{R_2 + R_4} \right)$$


$$-v_1 \left(\frac{1}{R_1} \right) + v_2 \left(\frac{1}{R_1} + \frac{1}{R_3} \right) - v_3 \frac{1}{R_3} + i_{s2} = 0 \text{ A}$$

Make a consistency check on the above node-voltage equations for the circuit by setting resistors and sources to values for which the values of v_1 , v_2 , and v_3 are obvious. State the values of resistors, sources, and v_1 , v_2 , v_3 for your consistency check, and show that the node-voltage equations are satisfied for these values. (In other words, plug the values into the node-voltage equations and show that they yield values of zero Amps.)

sol'n: Many consistency checks are possible.

One possible is to set $i_{s2} = 0A$
and $\alpha = 0$. Let $i_s = 6A$ and
set $R_1 = 1\Omega$, $R_2 = 2\Omega$, ..., $R_5 = 5\Omega$.

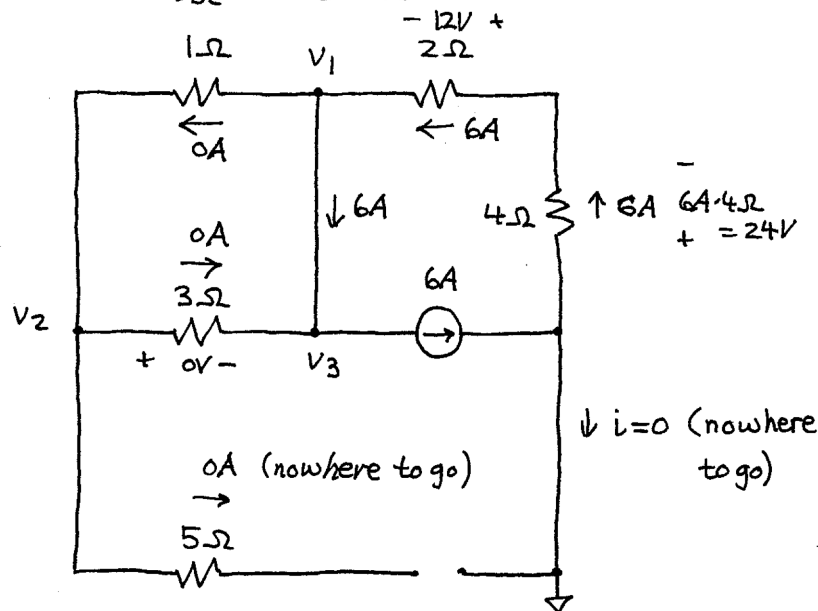With $\alpha = 0$, our v -src becomes a wire.
With $i_{s2} = 0A$ we have an open circuit
where i_{s2} is located.



All the current will flow thru the
wire between v_1 and v_3 , (path of least
resistance).

The 6A flows thru $R_2 + R_4$, giving
 v -drop of $6A \cdot (2\Omega + 4\Omega) = 36V$ from
reference to v_1 .

Thus, $v_1 = -36V$. $v_3 = v_1 = -36V$ (wire
connects v_1 to v_3)

Also, $v_2 = v_3 = -36V$ (0V across R_3 ; no current)

Now we plug our component values and v_1, v_2, v_3 values into the node-voltage eq'ns to see if the eq'ns are valid, (i.e. that left side of eq'n = right side of eq'n).

$$\begin{aligned}
 & -36V \left(\frac{1}{1\Omega} + \frac{1}{2\Omega + 4\Omega} \right) - (-36V) \left(\frac{1}{3\Omega} + \frac{1}{1\Omega} \right) + (-36V) \frac{1}{3\Omega} \\
 & \quad + 6A \\
 & = \cancel{-36A} - \cancel{6A} + \cancel{12A} + \cancel{36A} - \cancel{12A} + \cancel{6A} \\
 & = 0A \quad \text{eq'n satisfied } \checkmark
 \end{aligned}$$

Now we check 2nd eq'n.

$$\begin{aligned}
 & \cancel{-36V} - \cancel{(-36V)} \stackrel{?}{=} 0 \cdot \cancel{(-36V)} \frac{4\Omega}{2\Omega + 4\Omega} \xrightarrow{0} \\
 & \quad 0 = 0 \quad \checkmark
 \end{aligned}$$

Now we check 3rd eq'n.

$$\begin{aligned}
 & -(-36V) \left(\frac{1}{1\Omega} \right) + (-36V) \left(\frac{1}{1\Omega} + \frac{1}{3\Omega} \right) - (-36V) \frac{1}{3\Omega} + 0A \\
 & = \cancel{36A} - \cancel{36A} - \cancel{12A} + \cancel{12A} \\
 & = 0A \quad \checkmark
 \end{aligned}$$

This check worked. In practice we would perform others.