

a) Calculate  $i_\Delta$  and  $v_\sigma$ . Use Ohm's law, Kirchoff's laws.

Left-side V loop ( $\neq$  Ohm's law):  $12V - 2i_\sigma - i_\Delta 5\Omega = 0V$

Center V loop ( $\neq$  Ohm's law, as always):  $v_\sigma + 8i_\sigma - i_\Delta 5\Omega = 0V$

but  $v_\sigma = i_\sigma 2\Omega$  so center loop eq'n is:  $i_\sigma 2\Omega + 8i_\sigma - i_\Delta 5\Omega = 0V$

Now we have 2 eq'n's in two unknowns. Eliminate  $i_\sigma$ .


$$10i_\sigma - i_\Delta 5\Omega = 0 \quad (2nd \text{ eq'n}) \quad \therefore i_\sigma = i_\Delta \frac{5}{10} = \frac{i_\Delta}{2}$$

Substitute into 1st eq'n  $12V - \frac{2i_\Delta}{2} - i_\Delta 5\Omega = 0V$

$$i_\Delta = \frac{12V}{6\Omega} = 2A \quad (i_\sigma = 1A)$$

and  $v_\sigma = i_\sigma \cdot 2\Omega = \frac{i_\Delta}{2} \cdot 2\Omega = i_\Delta \cdot 1\Omega = 2V$

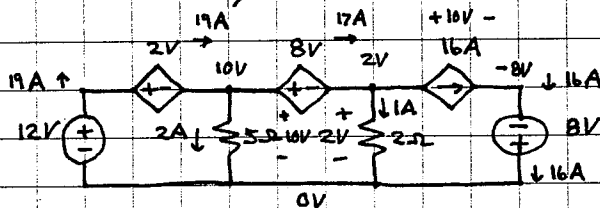Consistency check: put all  $i$ 's and  $v$ 's on circuit diagram and verify that it obeys Kirchoff's laws and Ohm's law.



Left loop  $V = 0$  and  $10V$  across  $5\Omega$  gives  $2A \checkmark$

Center loop  $V = 0$  and  $2V$  across  $2\Omega$  gives  $1A \checkmark$

b) Show power delivered = power absorbed for sol'n to (a).

Consistency check diagram for (a) shows  $v$ 's and  $i$ 's we get from solution plus what we deduce from Kirchoff's laws and Ohm's law. (We make sure total current into nodes = 0 and  $V$  drops around loops sum to 0V.)

An element develops power if positive current flows out of terminal labeled + for voltage. An element absorbs power if positive current flows into terminal labeled + for voltage. These definitions are for  $V_{drop} > 0$ . Reverse them if  $V_{drop} < 0$  from terminal labeled + to terminal labeled -.

element	power developed = $-i \cdot v$	power absorbed = $i \cdot v$
12V src	$19A \cdot 12V = 228W$	
2i <sub>g</sub> src		$19A \cdot 2V = 38W$
5Ω		$2A \cdot 10V = 20W$
8i <sub>g</sub> src		$17A \cdot 8V = 136W$
2Ω		$1A \cdot 2V = 2W$
8i <sub>A</sub> src		$16A \cdot 10V = 160W$
8V src	$16A \cdot 8V = 128W$	
	<hr/>	<hr/>
	tot 356W	tot 356W ✓