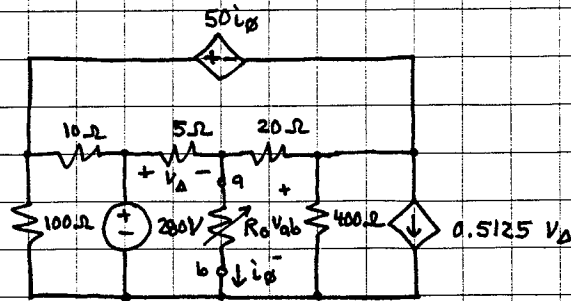


ex:



$R_o$  is adjusted for max power transfer to  $R_o$ .

a) Find the value of  $R_o$ .


sol'n: Take Thevenin equivalent of circuit without  $R_o$  with output a-b terminals as labeled in above diagram. Then set  $R_o = R_{Th}$ .

Find Thevenin equivalent:

$$V_{Th} = V_{ab} \text{ without } R_o \text{ (i.e. open circuit)}$$

Then  $i_φ = 0$  and  $50i_φ = 0V$  is wire.

Now use Node-V method:

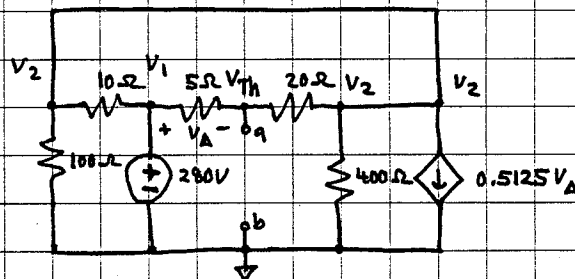

$V_{Th}$  not an essential node. Solve for  $V_1$  and  $V_2$ .  
Then use V-divider to find  $V_{Th}$ .

$V_1 = 280V$  since we have 280V source. So we really just need to find  $V_2$ .

$$\frac{V_2}{100\Omega} + \frac{V_2 - 280V}{10\Omega} + 0.5125V_A + \frac{V_2}{400\Omega} + \frac{V_2 - 280V}{5\Omega + 20\Omega} = 0A$$

constraint:  $V_A = (280 - V_2) \cdot \frac{5\Omega}{5\Omega + 20\Omega} = \frac{1}{5} (280 - V_2)$  (V-divider)

$$V_2 \left( \frac{1}{100\Omega} + \frac{1}{10\Omega} - \frac{41}{80} \frac{1}{5\Omega} + \frac{1}{400\Omega} + \frac{1}{25\Omega} \right) = 280V \left( \frac{1}{10\Omega} + \frac{1}{25\Omega} - \frac{1 \cdot 41}{5 \cdot 80\Omega} \right)$$

mult by 400Ω  $V_2 (4 + 40 - 41 + 1 + 16) = 280V (40 + 16 - 41)$

$$V_2 \cdot 20 = 280V \cdot 15$$


$$V_2 = 14 \cdot 15V = 210V$$

$$V_{Th} = 280V - V_A = 280V - \frac{(280 - 210)V \cdot 1}{5} = 266V$$

Now we find  $R_{Th}$ : Connect 1V source at a-b and turn independent 280V source to zero.

$$R_{Th} = 1V / (-i_{\phi}) \text{ since } i_{\phi} = -i_{1V} \text{ where } i_{1V} = i \text{ into 'a' terminal}$$

Circuit:

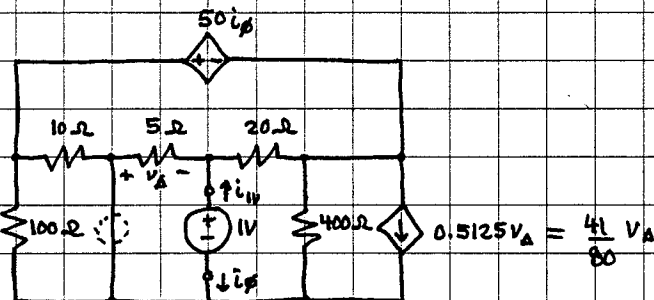


We observe that we have 1V source across 5Ω resistor.

$$\therefore V_A = -1V \quad \frac{41}{80} V_A = -\frac{41}{80} A$$

We also have  $10\Omega \parallel 100\Omega$  on left.

We also can transform  $400\Omega$  and  $0.5125V_A$  source to Thevenin equivalent:  $R = 400\Omega \quad V = -400 \cdot \frac{-41}{80} = +205V$

Time to redraw circuit.

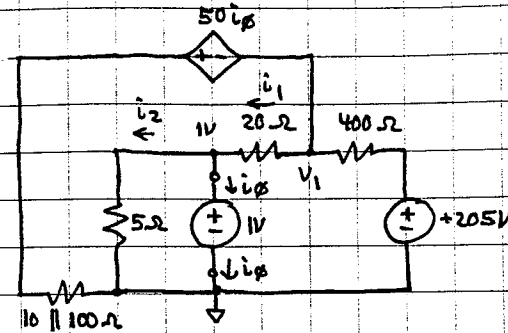

Use Node-v method to find  $v_1$ :

constraint:  $i_1 = i_2 + i_\phi$       $i_1 = \frac{v_1 - 1V}{20\Omega}$       $i_2 = \frac{1V}{5\Omega}$

$\therefore i_\phi = i_1 - i_2 = \frac{v_1 - 1V}{20\Omega} - \frac{1V}{5\Omega} = \frac{v_1 - 5V}{20\Omega}$

Node  $v_1$ :  $\frac{v_1 - 1V}{20\Omega} + \frac{v_1 - 205V}{400\Omega} + \frac{v_1 + 50i_\phi}{10 \parallel 100\Omega} = 0A$

$v_1 \left( \frac{1}{20\Omega} + \frac{1}{400\Omega} + \frac{1}{10 \parallel 100\Omega} + \frac{50/20}{10 \parallel 100\Omega} \right) = \frac{1V}{20\Omega} + \frac{205V}{400\Omega} + \frac{50 \cdot 5V}{20 \cdot 10 \parallel 100\Omega}$

mult by 400      $v_1 \left( 20 + 1 + \frac{400 \cdot 110}{1000} + \frac{50 \cdot 110 \cdot 400}{20 \cdot 1000 \cdot 50} \right) = \frac{20 + 205 + 250 \cdot 110 \cdot 400}{20 \cdot 1000} V$


$v_1 (20 + 1 + 44 + 110) = 20 + 205 + 550 V$

$v_1 \cdot 175 = 775V$

$i_{1V} = -i_\phi = \frac{v_1 - 5V}{20\Omega} = \frac{775V - 5V}{20\Omega}$

$R_{Th} = \frac{1V}{i_{1V}} = \frac{-20\Omega}{\frac{775 - 5}{175}} = 35\Omega$

Finally: Our equivalent circuit:

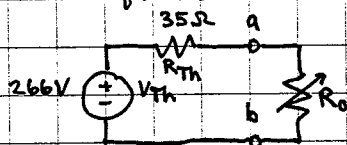

Max power to  $R_0$  when  $R_0 = R_{Th} = 35\Omega$

b) When  $R_o = R_{Th}$  the power delivered to  $R_o$  (i.e. the max power asked for, for part (b)) =  $\frac{V_{Th}}{2R_{Th}} \cdot \frac{V_{Th}}{2} = i \cdot v$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} \quad (\text{this formula always holds})$$

$$= \frac{266^2}{4 \cdot 35} \text{ W} = 505.4 \text{ W}$$

c) Find power delivered by 280V source when  $R_o$  adjusted for max power, (i.e.  $R_o = R_{Th} = 35\Omega$ , as above).

soln: We know  $V_{ab} = \frac{V_{Th}}{2} = 133V$ .


We also know  $i_s = \frac{V_{ab}}{R_o} = \frac{V_{Th}}{2R_o} = \frac{133V}{35\Omega}$

And  $\therefore V_{\Delta} = 280V - V_{ab} = 280 - 133V = 147V$

$$0.5125 V_{\Delta} = \frac{41}{80} V_{\Delta} = \frac{41}{80} \cdot 147V$$

$$50i_s = 50 \cdot \frac{133V}{35\Omega} = \frac{10 \cdot 133}{7} = \frac{10 \cdot 19.7}{7} = 190V$$

Circuit:

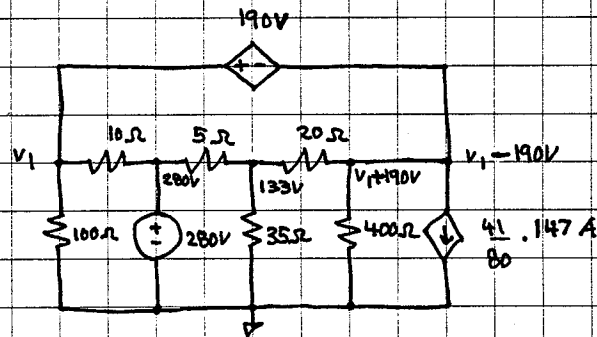

Use Node-V to find  $v_1$ :

$$\frac{v_1}{100\Omega} + \frac{v_1 - 280V}{10\Omega} + \frac{41 \cdot 147}{80} + \frac{v_1 - 190V}{400\Omega} + \frac{(v_1 - 190V) - 133V}{20\Omega} = 0A$$

$$v_1 \left( \frac{1}{100\Omega} + \frac{1}{10\Omega} + \frac{1}{400\Omega} + \frac{1}{20\Omega} \right) = \frac{280V}{10\Omega} - \frac{41 \cdot 147}{80} + \frac{190V}{400\Omega} + \frac{133V}{20\Omega}$$

$$\text{mult by } 400: \quad v_1 (4 + 40 + 1 + 20) = 280 \cdot 40 - 41 \cdot 147 \cdot 5 + 190 - 20 \cdot 323$$

$$v_1 \cdot 65 = 11200 - 30135 + 190 + 6460$$

$$v_1 = \frac{-12285}{65} = -189V$$

The current flowing out of the 280V source is:

$$i = \frac{280V - v_1}{10\Omega} + \frac{280 - v_{ab}}{5\Omega} = \frac{280 - (-189)}{10} + \frac{280 - 133}{5}$$

$$i = \frac{469}{10} + \frac{147}{5} = \frac{763}{10} = 76.3 \text{ A}$$

$$p = i \cdot V = 76.3 \text{ A} \cdot 280 \text{ V} = 21.364 \text{ kW}$$