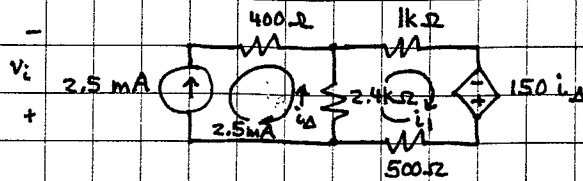


ex:



The mesh current for left loop = 2.5 mA from current source.

For the right loop:  $150 i_{\Delta} - i_1 \cdot 500 \Omega - (i_1 - 2.5 \text{ mA}) 2.4 \text{ k}\Omega - i_1 \cdot 1 \text{ k}\Omega = 0 \text{ V}$

Constraint eq'n for  $i_{\Delta}$ :  $i_{\Delta} = i_1 - 2.5 \text{ mA}$ . Use this in  $i_1$  loop eq'n.

$$150(i_1 - 2.5 \text{ mA}) - i_1 \cdot 500 \Omega - (i_1 - 2.5 \text{ mA}) 2.4 \text{ k}\Omega - i_1 \cdot 1 \text{ k}\Omega = 0 \text{ V}$$

$$\text{or } i_1 (150 \Omega - 500 \Omega - 2.4 \text{ k}\Omega - 1 \text{ k}\Omega) = 2.5 \text{ mA} \cdot (150 \Omega - 2.4 \text{ k}\Omega)$$

$$\text{or } i_1 = \frac{-2.5 \text{ mA} \cdot 2.25 \text{ k}\Omega}{-3.75 \text{ k}\Omega} = +1.5 \text{ mA}$$

a) We want  $i_{\Delta}$ :  $i_{\Delta} = i_1 - 2.5 \text{ mA} = 1.5 \text{ mA} - 2.5 \text{ mA} = -1 \text{ mA}$

b) Find pwr delivered by independent  $i$ -source: (i.e. 2.5 mA source)

$$\text{pwr delivered} = -i \cdot v_i = -2.5 \text{ mA} \cdot v_i$$

↑  
see diagram

$$v_i \text{ from loop } V_i \text{ sum to } 0 \text{ V: } -v_i - 2.5 \text{ mA} \cdot 400 \Omega + i_{\Delta} \cdot 2.4 \text{ k}\Omega = 0 \text{ V}$$

↑  
-1 mA

$$\text{or } v_i = -2.5 \text{ mA} \cdot 0.4 \text{ k}\Omega - 1 \text{ mA} \cdot 2.4 \text{ k}\Omega = -1 \text{ V} - 2.4 \text{ V} = -3.4 \text{ V}$$

$$\text{pwr delivered} = -2.5 \text{ mA} \cdot (-3.4 \text{ V}) = 8.5 \text{ mW}$$

c) Find pwr delivered by dependent source: (i.e.  $150 i_{\Delta}$ )

$$\text{pwr delivered} = i_1 \cdot 150 i_{\Delta} = 1.5 \text{ mA} \cdot 150 \Omega \cdot (-1 \text{ mA}) = -225 \mu\text{W}$$

$$\text{pwr absorbed} = -\text{pwr delivered} = 225 \mu\text{W}$$