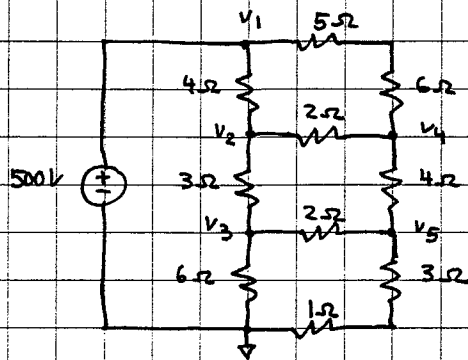


ex:



6 essential nodes
but v_1 is known
 \therefore we need $(6-1) - 1$ eqns
or 4 eqns for v_2, v_3, v_4, v_5

a) Use node-v to power in 5Ω R. Use Matlab.

We put ref at bottom of 500V, so we know $v_1 = 500V$.
 \therefore we don't need an eqn for v_1 .

$$\frac{v_2 - v_1}{4\Omega} + \frac{v_2 - v_4}{2\Omega} + \frac{v_2 - v_3}{3\Omega} = 0$$

$$\frac{v_3 - v_2}{3\Omega} + \frac{v_3 - v_5}{2\Omega} + \frac{v_3}{6\Omega} = 0$$

$$\frac{v_4 - v_1}{5\Omega + 6\Omega} + \frac{v_4 - v_2}{2\Omega} + \frac{v_4 - v_5}{4\Omega} = 0$$

$$\frac{v_5 - v_4}{4\Omega} + \frac{v_5 - v_3}{2\Omega} + \frac{v_5}{3\Omega + 1\Omega} = 0$$

Write as matrix

$$\begin{bmatrix} -1/4\Omega + 1/2\Omega + 1/3\Omega & -1/3\Omega & -1/2\Omega & 0/\Omega & v_2 = 500V/4\Omega \\ -1/3\Omega & 1/3 + 1/2 + 1/6\Omega & 0/\Omega & -1/2\Omega & v_3 = 0 \\ -1/2\Omega & 0/\Omega & 1/4 + 1/2 + 1/4\Omega & -1/4 & v_4 = 500V/11\Omega \\ 0/\Omega & -1/2\Omega & -1/4\Omega & 1/4 + 1/2 + 1/4\Omega & v_5 = 0 \end{bmatrix}$$

Now use Matlab to solve this matrix eqn.

From Matlab we get: $v_2 = 300\text{ V}$ $v_3 = 180\text{ V}$ $v_4 = 280\text{ V}$ $v_5 = 160\text{ V}$.

The power dissipated in the 5Ω Resistor is $i_5^2 \cdot 5\Omega$


$$\text{where } i_5 = \frac{v_4 - v_1}{5\Omega + 6\Omega} = \frac{280 - 500\text{ V}}{11\Omega} = \frac{-220\text{ V}}{11\Omega} = -20\text{ A}.$$

$$\therefore P_{5\Omega} = (-20)^2 \cdot 5\text{ W} = 2000\text{ W} \text{ or } 2\text{ kW}$$

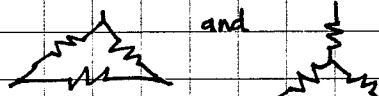b) Find the power supplied by 500 V source.


We might be tempted to calculate the equivalent resistance, R_{eq} , for all the resistors in the diagram and then use $P_{500} = (500\text{ V})^2 / R_{eq}$.

Unfortunately, we would have to deal with Δ and Y configurations:



We would need results from text, section 3.7. This approach would also be very tedious.

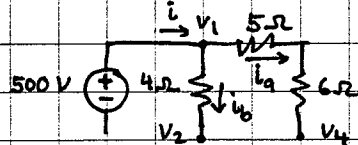Instead, we just note that current i flowing out of the 500 V source must equal the currents thru the 5Ω and 4Ω R's connected to node v_1 : $i = i_a + i_b$



$$i_a = \frac{v_1 - v_4}{5\Omega + 6\Omega} \quad i_b = \frac{v_1 - v_2}{4\Omega}$$

$$\text{or } i_a = \frac{500 - 280\text{ V}}{11\Omega} = \frac{220\text{ V}}{11\Omega} = 20\text{ A} \quad i_b = \frac{500 - 300\text{ V}}{4\Omega} = \frac{200\text{ V}}{4\Omega} = 50\text{ A}$$

$$\therefore i = 20\text{ A} + 50\text{ A} = 70\text{ A}$$

$$P_{500\text{V}} = i \cdot 500\text{ V} = 70\text{ A} \cdot 500\text{ V} = 35000\text{ W} \text{ or } 35\text{ kW}$$