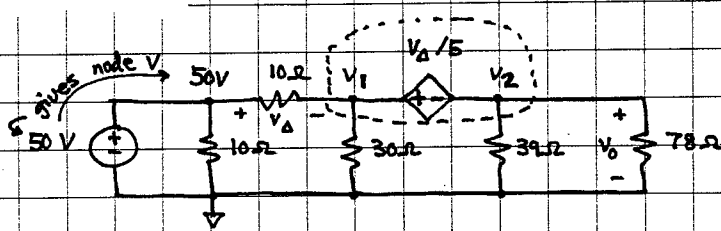


ex:



Use Node-Voltage method to find  $V_0$ .

Obvious place to put ref is at bottom of circuit.

We know we have 50V at top-left node.  $\therefore$  only 2 nodes unknown

Use the idea of a supernode: currents flowing out of dashed box in above figure sum to zero, and the controlled  $V$ -source gives us  $V_1 - V_2 = V_\Delta / 5$ .

$$\text{Super-Node 1\&2: } \frac{V_1 - 50V}{10\Omega} + \frac{V_1 - 0V}{30\Omega} + \frac{V_2 - 0V}{39\Omega} + \frac{V_2 - 0V}{78\Omega} = 0A$$

$$V_1 - V_2 = V_\Delta / 5 \quad \text{from } V\text{-source inside supernode}$$

$$-V_\Delta = V_1 - 50V \quad \text{from definition of } V_\Delta \text{ on schematic}$$

We have 3 eqs in 3 unknowns. Eliminate  $V_\Delta$ . Then find  $V_2$  by eliminating  $V_1$ . Why? because we want to find  $V_0$ , but  $V_0 = V_2$ .

$$\text{Using } -V_\Delta = V_1 - 50V \text{ in 2nd eqn: } V_1 - V_2 = \frac{-(V_1 - 50V)}{5}$$

$$\therefore V_2 = V_1 + \frac{V_1 - 50V}{5} = \frac{6}{5} V_1 - 10V \Rightarrow V_1 = \frac{5}{6} (V_2 + 10V)$$

$$\text{Plug this into 1st eqn: } \frac{5}{6} (V_2 + 10V) \left( \frac{1}{10\Omega} + \frac{1}{30\Omega} \right) + V_2 \left( \frac{1}{39\Omega} + \frac{1}{78\Omega} \right) = \frac{50V}{10\Omega}$$

$$\frac{1}{10\Omega} + \frac{1}{30\Omega} = \frac{1}{10\Omega \parallel 30\Omega} = \frac{1}{10\Omega \parallel 30\Omega} = \frac{4}{30\Omega}$$

$$\frac{1}{39\Omega} + \frac{1}{78\Omega} = \frac{1}{39\Omega \parallel 78\Omega} = \frac{1}{39\Omega \parallel 78\Omega} = \frac{3}{78\Omega} \quad \therefore \frac{5}{6} (V_2 + 10V) \frac{4}{30\Omega} + V_2 \frac{3}{78\Omega} = 5A$$

$$V_2 \left( \frac{5 \cdot 4}{6 \cdot 30\Omega} + \frac{3}{78\Omega} \right) = 5A - \frac{5 \cdot 10V}{6 \cdot 30\Omega} \quad \therefore V_0 = V_2 = \frac{35/9 \cdot (A \cdot \Omega = V)}{1/9 + 3/78}$$

$$\text{or } V_0 = 26V$$