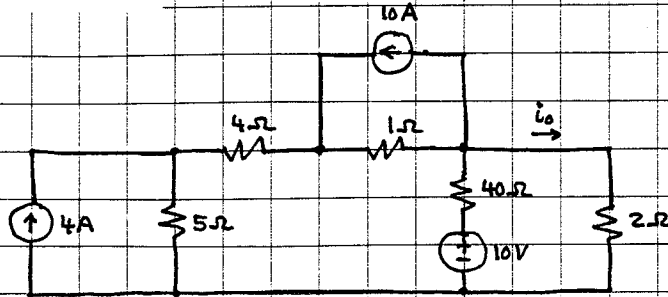



ex:



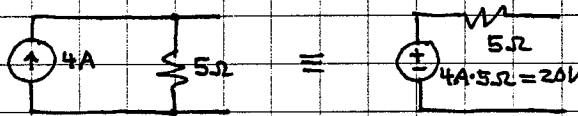
a) Find  $i_o$  using source transformations.

Note: We must avoid any transformations that would cause  $i_o$  to end up inside the transformed components, (or we change  $i_o$ ). Thus, we work from left to right.



Transform 4A & 5Ω on left to Thevenin equivalent:



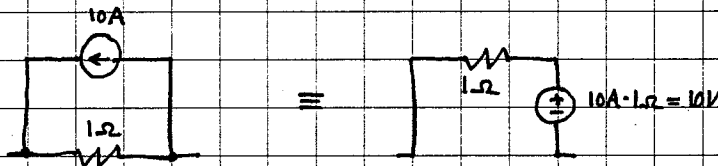
Transform 10A & 1Ω on top to Thevenin equivalent:




Now our circuit is:

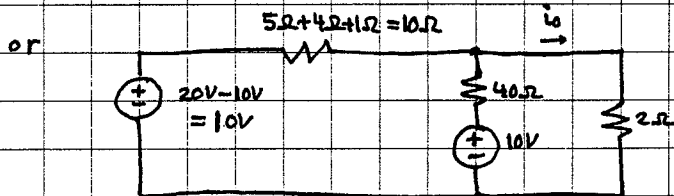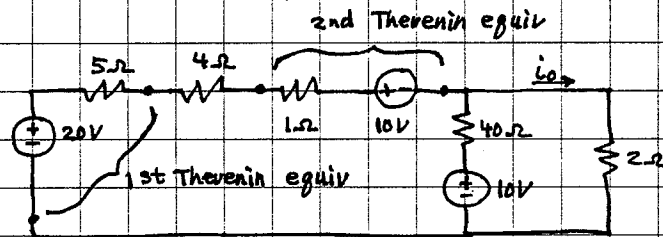

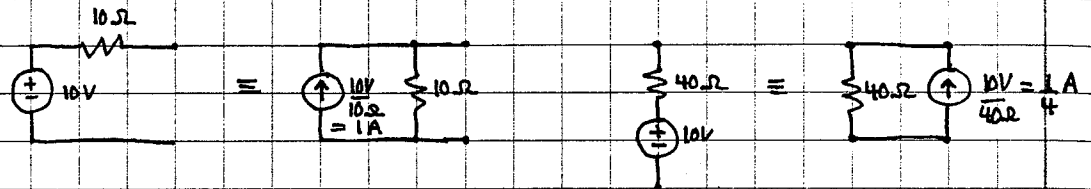
Transform the  $10V, 10\Omega$  to Norton equivalent, and  
 " "  $10V, 40\Omega$  " " " "



Now we have the following circuit:

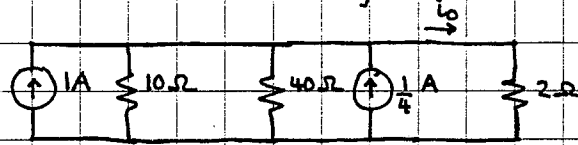

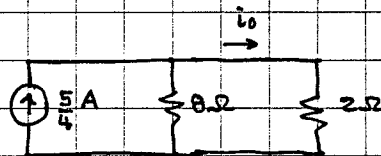Add the current sources; use parallel resistance  $10\Omega \parallel 40\Omega = 10\Omega \left( \frac{4}{4} \right) = 10 \cdot \frac{4}{5} \Omega = 8\Omega$   
 $1A + \frac{1}{4}A = \frac{5}{4}A$



Now we have current divider:  $i_o = \frac{8\Omega}{2\Omega + 8\Omega} \cdot \frac{5}{4}A = \frac{8 \cdot 5}{10} \frac{A}{4} = 1A$