

a) Compute  $V_s$  and  $V_L$

b) Construct phasor diagram showing  $V_s$ ,  $V_L$ , and  $440\angle 0^\circ V$ .

c) Repeat (a) and (b) with added capacitive load (and with  $440\angle 0^\circ V$  still).

a) sol'n: Use V-divider formula  $440\angle 0^\circ V = V_s \frac{22\Omega \parallel j22\Omega}{22\Omega \parallel j22\Omega + 0.2\Omega + j1.6\Omega}$

$$22\Omega \parallel j22\Omega = 22\Omega \cdot \frac{1 \parallel j}{1+j} = 22\Omega \frac{j}{1+j} = 22\Omega \frac{j}{1+j} \frac{1-j}{1-j} = 22\Omega \frac{1+j}{2}$$

$$= 11\Omega \cdot (1+j)$$

$$\therefore 440\angle 0^\circ V = V_s \frac{11\Omega \cdot (1+j)}{11\Omega \cdot (1+j) + 0.2 + j1.6\Omega} = V_s \frac{11\Omega (1+j)}{11.2\Omega + j12.6\Omega}$$

$$\text{or } V_s = 440 V \cdot \frac{11.2 + j12.6 \Omega}{11 (1+j) \Omega} = \frac{440}{11} \frac{(11.2 + j12.6)(1-j)}{(1+j)}$$


$$= 40 \frac{11.2 + 12.6 + j(-11.2 + 12.6)}{2} = 20 (23.8 + j1.4) V$$

$$= 476 + j28 V = 476.8 \angle 3.37^\circ V$$

$$V_L = V_s - 440\angle 0^\circ V = 476 + j28 - 440 V = 36 + j28 V$$

$$= 36 + j28 V = 45.6 \angle 37.87^\circ V$$

b) sol'n:

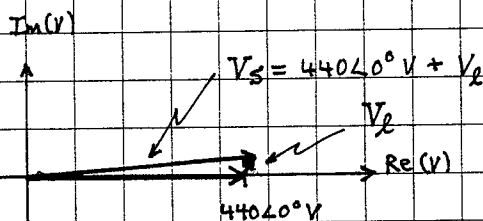

The phasor diagram shows  $440\angle 0^\circ V$ ,  $V_L$ , and  $V_s$  as vectors, and it shows that  $440\angle 0^\circ V + V_L = V_s$ .

c) sol'n: With added load we have  $22\Omega \parallel j22\Omega \parallel (-j22)\Omega$ .

In situations like this, we avoid a divide by zero if we use  $R_1 \parallel R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$  instead of  $R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$ .

$$22\Omega \parallel j22\Omega \parallel -j22\Omega = 22\Omega \cdot \frac{1}{\frac{1}{1} + \frac{1}{j} + \frac{1}{-j}} = 22\Omega$$

The L and the C cancel each other...

For sake of illustration, we take a different approach than previous sol'n. (Previous approach would still work.)

Define  $I = \frac{440\angle 0^\circ V}{22\Omega}$ .  $V_s = 440\angle 0^\circ V + I \cdot (0.2 + j1.6)\Omega$

$$\therefore V_s = 440 \left(1 + \frac{1}{22} (0.2 + j1.6)\right) V = 440 \cdot \frac{22.2 + j1.6}{22} V$$

$$V_s = 20 (22.2 + j1.6) V = 444 + j32 V = 445.15 \angle 4.12^\circ V$$

$$V_s = 440\angle 0^\circ V + V_L \Rightarrow V_L = 4 + j32 V = 32.25 \angle 82.87^\circ V$$

