



- a) Find cutoff frequency (Hz) for above high-pass filter.
 b) Find $H(j\omega)$ for $\omega = \omega_c$, $0.1\omega_c$, and $10\omega_c$.
 c) Given $v_i = 800 \cos \omega t$ mV, find $v_o(t)$ for $\omega = \omega_c$, $0.1\omega_c$, $10\omega_c$.

ans: a) $f_c = 1590$ Hz

b) $H(j\omega_c) = \frac{1}{\sqrt{2}} \angle 45^\circ$, $H(j0.1\omega_c) = 99.5 \angle 84.3^\circ$ m, $H(j10\omega_c) = 0.995 \angle 5.71^\circ$

c) $v_o(\omega_c) = 566 \cos(10kt + 45^\circ)$ mV
 $v_o(0.1\omega_c) = 79.6 \cos(1kt + 84.3^\circ)$ mV
 $v_o(10\omega_c) = 796 \cos(100kt + 5.71^\circ)$ mV

sol'n a) As noted in sol'n to 14.1, the cutoff frequency for a high-pass or low-pass is where $\text{Re}[H(j\omega)] = \text{Im}[H(j\omega)]$.

Our transfer function $H(j\omega) = \frac{V_o}{V_i}$.

$V_o = V_i \cdot \frac{R}{R + 1/j\omega C}$ V-divider $\therefore H(j\omega) = \frac{V_o}{V_i} = \frac{R}{R + 1/j\omega C}$

$H(j\omega) = \frac{j\omega RC}{1 + j\omega RC} = \frac{j\omega RC}{1 + j\omega RC} \frac{1 - j\omega RC}{1 - j\omega RC} = \frac{(\omega RC)^2 + j\omega RC}{1 + (\omega RC)^2}$

Denominator is real, so solve for real part of numerator = imaginary part of numerator.

$(\omega_c RC)^2 = \omega_c RC$ or $\omega_c RC = 1$ or $\omega_c = \frac{1}{RC}$

$f_c = \frac{\omega_c}{2\pi} = \frac{1}{2\pi RC} = \frac{1}{2\pi \cdot 40k \cdot 2.5n} = \frac{1M}{2\pi \cdot 100} = \frac{10k}{2\pi}$ Hz

$f_c = 1590$ Hz

b) Use $H(j\omega)$ from part (a).

$$RC = 40k \cdot 2.5n = 100\mu \text{ (but always cancels)}$$

$$H(j\omega_c) = \frac{\left(\frac{1}{RC}\right)^2 + j \frac{1}{RC} RC}{1 + \left(\frac{1}{RC} RC\right)^2} = \frac{1+j}{1+1} = \frac{1}{2} + j\frac{1}{2}$$

$$" = \sqrt{\left(\frac{1}{2}\right)^2 + \left(\frac{1}{2}\right)^2} \angle \tan^{-1} \frac{1/2}{1/2} = \frac{1}{\sqrt{2}} \angle 45^\circ$$

$$H(j0.1\omega_c) = \frac{(0.1)^2 + j0.1}{1 + (0.1)^2} = \frac{0.01 + j0.1}{1.01} = \frac{0.01 + j0.1}{1.01}$$

$$" = \frac{\sqrt{(0.01)^2 + (0.1)^2}}{1.01} \angle \tan^{-1} \frac{0.1}{0.01} = 99.5 \angle 84.3^\circ \text{ m}$$

can ignore real denominator
if it's positive

$$H(j10\omega_c) = \frac{10^2 + j10}{1 + 10^2} = \frac{100 + j10}{101}$$

$$" = \frac{\sqrt{100^2 + 10^2}}{101} \angle \tan^{-1} \frac{10}{100} = 0.995 \angle 5.71^\circ$$

c) Phasor $V_o = V_i \cdot H(j\omega)$

$$v_i(t) = 800 \cos \omega t \text{ mV} \xrightarrow{PC} V_i = 800 \angle 0^\circ \text{ mV}$$

$$V_o(\omega_c) = 800 \angle 0^\circ \text{ mV} \cdot \frac{1}{\sqrt{2}} \angle 45^\circ = 566 \angle 45^\circ \text{ mV}$$

$$v_o(t) \text{ for } \omega = \omega_c = 566 \cos(\omega t + 45^\circ) \text{ mV}$$

$$V_o(0.1\omega_c) = 800 \angle 0^\circ \text{ mV} \cdot 99.5 \angle 84.3^\circ \text{ m} = 79.6 \angle 84.3^\circ \text{ mV}$$

$$v_o(t) \text{ for } \omega = 0.1\omega_c = 79.6 \cos(\omega t + 84.3^\circ) \text{ mV}$$

$$V_o(10\omega_c) = 800 \angle 0^\circ \text{ mV} \cdot 0.995 \angle 5.71^\circ = 796 \angle 5.71^\circ \text{ mV}$$

$$v_o(t) \text{ for } \omega = 10\omega_c = 796 \cos(\omega t + 5.71^\circ) \text{ mV}$$