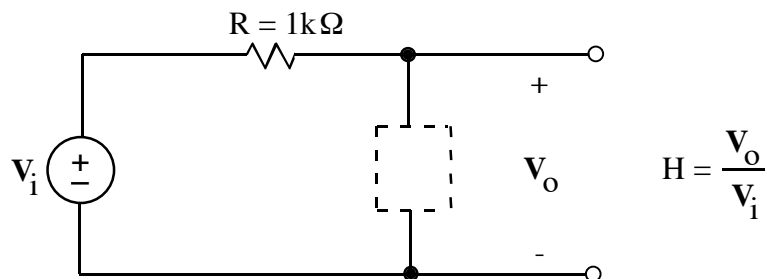


EX: Choose one R, one L, or one C to go in the box to make the circuit a high-pass filter with a cutoff frequency $\omega_c = 10^5$ r/s. Give the value of the element you chose.



ANS: $L = 10$ mH

SOL'N: The output of the filter is given by the voltage divider formula, rearranged to express the transfer function $H(\omega)$:

$$H(j\omega) \equiv \frac{V_o}{V_i} = \frac{z}{R + z} \quad \text{where } z \text{ is impedance in box}$$

For high-pass, we want $|H(j\omega)| = 0$ for $\omega = 0$. So we want $z = 0$ at $\omega = 0$.

$$\therefore \text{Choose } L \text{ so } z = j\omega L \text{ and } H(j\omega)|_{\omega=0} = \frac{0}{R} = 0.$$

The resulting transfer function is

$$H(j\omega) = \frac{j\omega L}{R + j\omega L}$$

ω_c is ω where $\text{denom } R = \omega L$, i.e. $\text{Re}[\text{denom}] = \text{Im}[\text{denom}]$.

$$\therefore \omega_c = \frac{R}{L} \Rightarrow L = \frac{R}{\omega_c} = \frac{1 \text{ k}}{100 \text{ k}} = 10 \text{ mH}$$