
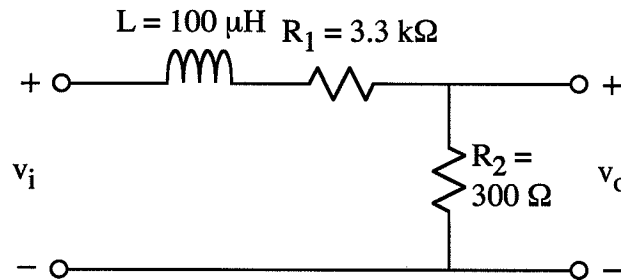


Ex:

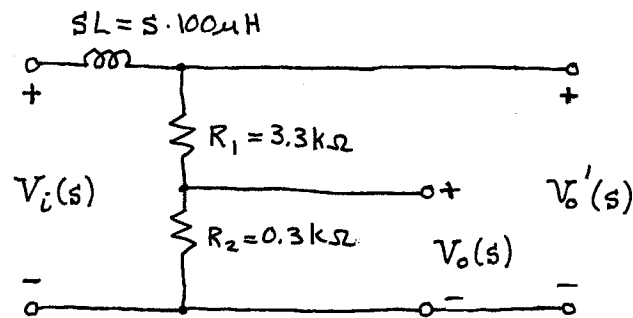

- Determine the transfer function V_o/V_i . **Hint:** Suppose the output were tapped from the point between L and R_1 . Then use a voltage divider.
- Plot $|V_o/V_i|$ versus ω .
- Find the cutoff frequency, ω_c .

sol'n: a) Consider tapping the output from between L and R_1 . Then use a V -divider to relate v_o to the voltage between L and R_1 .



$$V_o(s) = V_o'(s) \frac{R_2}{R_1 + R_2}$$

Using the V -divider formula, we have

$$V_o = V_i (R_1 + R_2) / (R_1 + R_2 + sL)$$

Thus,
$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{R_2}{R_1 + R_2} \frac{R_1 + R_2}{R_1 + R_2 + sL}$$

$$H(s) = \frac{R_2}{R_1 + R_2 + sL}$$

b) $|V_o/V_i| \equiv |H(s)|$

$sL = 0$ at $\omega = 0 \Rightarrow L = \text{wire}$ at $\omega = 0$

Thus, for $\omega = 0$, we have a simple V-divider.


$$|H(s=j\omega)| = \frac{R_2}{R_1 + R_2}$$

$sL \rightarrow \infty$ as $\omega \rightarrow \infty \Rightarrow L = \text{open}$ as $\omega \rightarrow \infty$

Thus, the output is disconnected from the input and $|H(s)| \rightarrow 0$ as $\omega \rightarrow \infty$.

$|H(s)|$ decreases as ω increases since

$$|R_1 + R_2 + sL| = \sqrt{(R_1 + R_2)^2 + (\omega L)^2} \text{ increase with } \omega.$$

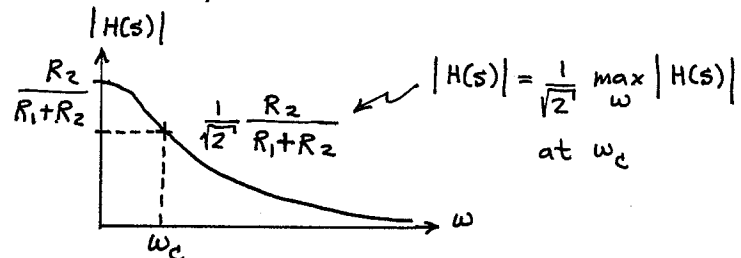

We find ω_c below.

c) ω_c is the ω where $|H(s)|$ is reduced by a factor of $\sqrt{2}$ relative to $\max_{\omega} |H(s)|$.

$$\text{Thus, } |H(s=j\omega_c)| = \frac{1}{\sqrt{2}} \max_{\omega} |H(s)| = \frac{1}{\sqrt{2}} \frac{R_2}{R_1+R_2},$$

$$\text{or } \left| \frac{R_2}{R_1+R_2+j\omega_c L} \right| = \frac{1}{\sqrt{2}} \frac{R_2}{R_1+R_2}.$$

We write $H(s)$ in the form $k \frac{1}{1+jX}$

where $k \equiv$ real constant, $X \equiv$ real expression

$$H(s) = \frac{R_2}{R_1+R_2} \frac{1}{1+j\omega_c \frac{L}{R_1+R_2}}$$

$$|H(s)| = \frac{R_2}{R_1+R_2} \cdot \frac{1}{\left| 1+j\omega_c \frac{L}{R_1+R_2} \right|}$$

$$\text{Thus, we have } \frac{R_2}{R_1+R_2} \frac{1}{\left| 1+j\frac{L}{R_1+R_2}\omega_c \right|} = \frac{R_2}{R_1+R_2} \frac{1}{\sqrt{2}}$$

$$\text{So } \left| 1+j\frac{L}{R_1+R_2}\omega_c \right| = \sqrt{2}.$$

$$\text{The solution is } 1+j\frac{L\omega_c}{R_1+R_2} = 1 \pm j,$$

$$\text{since } |1 \pm j| = \sqrt{2}. \text{ We must have } \frac{L\omega_c}{R_1+R_2} = 1.$$

$$\text{Thus, } \omega_c = \frac{R_1+R_2}{L} = \frac{3.3\text{k}\Omega + 0.3\text{k}\Omega}{100\mu\text{H}}$$

$$\omega_c = \frac{3.6\text{k}\Omega}{100\mu\text{H}} = 36 \text{ M r/s}$$