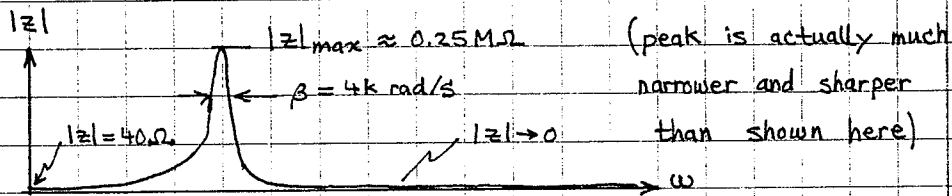


Plot  $|Z|$  and determine how  $|Z|$  depends (qualitatively) on  $R$ ,  $L$ , and  $C$ .

ans: (plot)



sol'n:

$$Z = (Z_L + Z_R) \parallel Z_C = (j\omega L + R) \parallel \frac{1}{j\omega C}$$

$$= \frac{j\omega L + R}{j\omega C} = \frac{L}{C} + \frac{R}{j\omega C}$$

$$\frac{j\omega L + R + \frac{1}{j\omega C}}{j\omega C} = \frac{R + j(\omega L - \frac{1}{\omega C})}{j\omega C}$$

$$= \frac{L}{C} \frac{(1 + \frac{R}{j\omega L})}{R + j(\omega L - \frac{1}{\omega C})} = \frac{L}{RC} \frac{(1 - j \frac{R}{L} \frac{1}{\omega})}{1 + j(\omega \frac{L}{R} - \frac{1}{\omega RC})}$$

The last expression for  $Z$  is convenient for several reasons:


- 1) The numerator and denominator are both of form  $1 \pm jW$  where  $W$  is a real quantity. In other words, the real part is one, and we can compare the magnitude of the real and imaginary parts by comparing 1 and  $W$ .
- 2)  $\omega$  only appears in the imaginary parts of the numerator and denominator.
- 3) All the coefficients multiplying  $\omega$  are time constants.
- 4) The scaling factor of  $\frac{L}{RC}$  out front gives us some information about the dependence of  $Z$  on each component value.

Before proceeding further, we observe the following:

- 1) For  $\omega = 0$   $j\omega L = 0$  and  $1/j\omega C = \infty$

Thus, we have


$$z = R = 40 \Omega$$

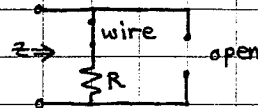

- 2) For  $\omega \rightarrow \infty$   $j\omega L = \infty$  and  $1/j\omega C = 0$


Thus, we have

$$z = 0 \Omega$$

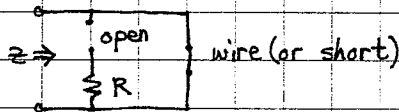

- 3) Since we have an RLC circuit, we might get a resonant peak or dip at the resonant frequency

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10m \cdot 1000p}} = \frac{1}{\sqrt{10}} \text{ M rad/s.}$$

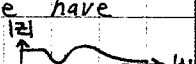We expect a peak (rather than a dip) because we already know that  $z \rightarrow 0$  as  $\omega \rightarrow \infty$ , and we have never seen an RLC response vs  $\omega$  of form . In other words,  $|z|$  would have too many wiggles.

At  $\omega_0 = \frac{1}{\sqrt{LC}}$ , we have  $\text{Im}[\text{Denominator of } z] = 0$ .

This condition helps to make  $z$  larger. But we also have an  $\omega$  dependence in the numerator that may shift the frequency where the max of  $|z|$  occurs.

To find  $\omega_p$  where  $\max_{\omega} |z|$  occurs, we could use  $\frac{d}{d\omega} |z| = 0$  at  $\omega_p$ . Then we could solve for  $\omega_p$ .

There is a simpler approach, however. We may be able to argue that  $\omega_p \approx \omega_0$ . If so, we save a lot of work!

We will need to know the following values in our upcoming calculations and approximations:

$$\frac{L}{R} = \frac{10\text{m}}{40} = \frac{1}{4} \text{ms} \quad \& \quad \frac{R}{L} = 4\text{k}/\text{s}$$

$$RC = 40 \cdot 1\text{kp} = 40\text{ns} \quad \& \quad \frac{1}{RC} = \frac{1}{40} \text{G}/\text{s} = 25\text{M}/\text{s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10\text{m} \cdot 1\text{kp}}} = \frac{1\text{M}}{\sqrt{10}} \text{rad}/\text{s} \quad \& \quad \sqrt{LC} = \sqrt{10} \mu\text{s} = \frac{1}{\omega_0}$$

Now consider  $\omega = \omega_0$ . We have:

$$z|_{\omega_0} = \frac{\frac{L}{RC} \left( 1 - j \frac{R}{L} \frac{1}{\omega_0} \right)}{1 + j \cdot 0} = \frac{L}{RC} \left( 1 - j \frac{R}{L} \frac{1}{\omega_0} \right)$$

$$= \frac{L}{RC} - j \frac{1}{C} \frac{1}{\omega_0} = \frac{1}{C} \left( \frac{L}{R} - \frac{j}{\omega_0} \right)$$

$$= \frac{1}{C} \left( \frac{1}{4} \text{ms} - j \sqrt{10} \mu\text{s} \right)$$

$\uparrow$  much smaller than real part

$$\approx \frac{1}{C} \frac{1}{4} \text{ms} = \frac{1}{1\text{kp}} \frac{1}{4} \text{ms} = \frac{1}{4} \text{M}\Omega$$

Note how the imaginary part was small and could be ignored. This suggests that, when we look for the  $\omega$  where  $\max_{\omega} |z|$  occurs, the imaginary part of the numerator probably doesn't move the  $\omega_p$  for  $\max |z|$  very far from  $\omega_0 = 1/\sqrt{LC}$ .

To prove  $\omega_p \approx \omega_0$ , we show that a small change in  $\omega$ , when  $\omega \approx \omega_0$ , will cause a large increase in  $|$ denominator of  $z|$  and only a small increase in  $|$ numerator of  $z|$ . Thus,  $|z|$  would go down for  $\omega \neq \omega_0$ .

$$\text{At } \omega_0, \quad \frac{R}{L} \frac{1}{\omega} = \frac{4 \text{ k}\Omega / \text{s}}{1 \text{ M/s}} = 4 \sqrt{10} \text{ m} \ll 1,$$

$$\text{and } \frac{L}{R} \omega = \frac{1 \text{ k}}{4 \sqrt{10}} \gg 1,$$

$$\text{and } \frac{1}{\omega RC} = \frac{1}{1 \text{ M/s} \cdot 40 \text{ k}\Omega} = \frac{\sqrt{10} \text{ k}}{40} = \frac{1 \text{ k}}{4 \sqrt{10}} \gg 1.$$

To show that the magnitude of the denominator of  $|z|$  changes faster than the numerator of  $|z|$ , we use derivatives.

$$|z| = \frac{L}{RC} \frac{\left| 1 - j \frac{R}{L} \frac{1}{\omega} \right|}{\left| 1 + j \left( \frac{\omega L}{R} - \frac{1}{\omega RC} \right) \right|} = \frac{L}{RC} \frac{\sqrt{1^2 + \left( \frac{R}{L} \frac{1}{\omega} \right)^2}}{\sqrt{1^2 + \left( \frac{\omega L}{R} - \frac{1}{\omega RC} \right)^2}}$$

$$\text{Numerator: } \frac{d}{d\omega} \left. \frac{R}{L} \frac{1}{\omega} \right|_{\omega_0} = \frac{R}{L} \left. \left( -\frac{1}{\omega^2} \right) \right|_{\omega_0} = \frac{40}{10 \text{ m}} \frac{-1}{\left( 1 \text{ M} \right)^2} = -40 \text{ ns}$$

$$\begin{aligned} \text{Denominator: } \frac{d}{d\omega} \left. \left( \frac{\omega L}{R} - \frac{1}{\omega RC} \right) \right|_{\omega_0} &= \left. \frac{L}{R} + \frac{1}{RC \omega^2} \right|_{\omega_0} \\ &= \frac{10 \text{ m}}{40} + \frac{1}{40 \text{ n} \left( 1 \text{ M} \right)^2} = \frac{1 \text{ m}}{4} + \frac{1 \text{ m}}{4} \text{ s} \\ &= \frac{1}{2} \text{ ms} \end{aligned}$$

The magnitude of the denominator change for a small change in  $\omega$  is clearly much larger than the magnitude of the numerator change. We conclude that moving away from  $\omega_0$  will lower  $|z|$ .  $\therefore \omega_p \neq \omega_0$

Note: The minus sign in numerator derivative just means the numerator increases if  $\omega$  decreases.

From the above discussion, we conclude that we may approximate  $z$  for  $\omega \approx \omega_0$  as follows:

$$z|_{\omega \approx \omega_0} \approx \frac{L/RC}{1 + j\left(\omega \frac{L}{R} - \frac{1}{\omega RC}\right)}$$

Now we can find the "bandwidth" of the peak in  $|z|$ .

We solve  $|z| = \frac{1}{\sqrt{2}} \cdot |z|_{\omega=\omega_0}$  =  $\frac{1}{\sqrt{2}} L/RC$   
i.e.  $\max_{\omega} |z|$  (approximately)

$$|z| \approx \frac{L/RC}{\sqrt{1^2 + \left(\omega \frac{L}{R} - \frac{1}{\omega RC}\right)^2}} = \frac{1}{\sqrt{2}} \frac{L}{RC}$$

$$\text{or } 1^2 + \left(\omega \frac{L}{R} - \frac{1}{\omega RC}\right)^2 = 2$$

$$\text{or } \left(\omega \frac{L}{R} - \frac{1}{\omega RC}\right)^2 = 1^2$$

$$\text{or } \omega \frac{L}{R} - \frac{1}{\omega RC} = \pm 1$$

$$\text{or } \omega^2 \frac{L}{R} - \frac{1}{RC} = \pm \omega$$

$$\text{or } \omega^2 \pm \frac{R}{L} \omega - \frac{1}{LC} = 0$$

$$\omega_{1,2} = \mp \frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\text{and } \beta \equiv \omega_{c2} - \omega_{c1} = \frac{R}{L} = \frac{40}{10m} = 4 \text{ krad/s}$$

Summary:  $\max_{\omega} |z| \approx \frac{L}{RC}$        $\beta \approx \frac{R}{L}$

$$|z|_{\omega=0} = R \quad |z|_{\omega \rightarrow \infty} = 0$$