
Fourier Series Circuit response Ex 2

Ex:

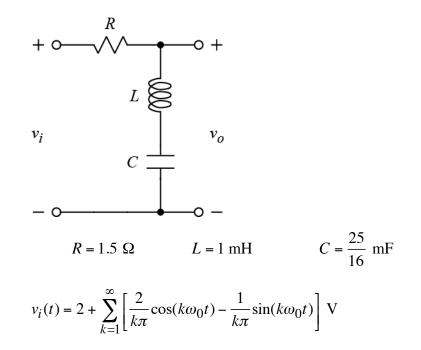

Write the time-domain expression of the first harmonic (i.e., k = 1) of  $v_0(t)$ . Note:  $\omega_0 = 3.2$  k r/s for the Fourier series.

SOL'N: The k=1 term of  $v_i(t)$  does not include the DC term,  $a_V = zv$ , since the DC term has frequency zero rather than  $w_0$ .  $v_{il}(t) = \frac{2}{\pi} \cos(w_0 t) - \frac{1}{\pi} \sin(w_0 t)$ Now we convert to a phasor. Note that  $P[\cos(w_0 t)] = 1$  and  $P[\sin(w_0 t)] = -j$ .  $V_{il} = \frac{2}{\pi} - -j\frac{1}{\pi} = \frac{1}{\pi}(2+j)$ The output phasor for frequency  $w_0$  may be obtained by a roltage-divider or by multiplying  $V_{il}$  by transfer function H(jw) evaluated at  $w = w_0$ .

FOURIER SERIES CIRCUIT RESPONSE Ex 2 (cont.)

 $+ \circ \psi_{jwL} = 0 + j_{wL} = v_{o}$  $v_{i} = \frac{1}{jwC} = v_{o}$  $H(j\omega) = \frac{j\omega L + \frac{1}{j\omega C}}{R + j\omega L + L}$  $= \frac{1}{\frac{R}{j\omega L + 1}} + 1$ jwC  $= \frac{1}{1 + \frac{R}{j(\omega L - \frac{1}{\omega C})}}$  $H(jw) = \frac{1}{1 - j \frac{R}{wL - 1}}$ wd H(iwa)

$$l(j\omega_{o}) = \frac{1}{1-j \frac{R}{\omega_{o}L - \frac{1}{\omega_{o}C}}}$$

where

R= 1.5 1 woL = 3.2 kr/s. 1 mH = 3.2 1

$$\frac{1}{w_{o}C} = \frac{1}{3.2 \text{ kr/s} 25 \text{ mF}} = \frac{1}{5} \Omega = 0.2 \Omega$$

Thus,  $\frac{R}{w_{o}L - \frac{L}{\omega_{o}C}} = \frac{1.5 \Omega}{3.2 \Omega - 0.2 \Omega} = \frac{1.5 \Omega}{3 \Omega} = \frac{1}{2}$ .

FOURIER SERIES CIRCUIT RESPONSE Ex 2 (cont.)

We have 
$$V_{01} = V_{i1} H(jw_0)$$
  

$$= \frac{1}{\pi} (2+j) V \frac{1}{1-j\frac{1}{2}}$$

$$= \frac{1}{\pi} (2+j) V \frac{1}{1-j\frac{1}{2}} \frac{1+j\frac{1}{2}}{1+j\frac{1}{2}}$$

$$= \frac{1}{\pi} (2+j) (1+j\frac{1}{2}) V$$

$$= \frac{1}{\pi} (2-j\frac{1}{2}+j+j) / \frac{5}{4} V$$

$$= \frac{1}{\pi} (\frac{3}{2}+j2) \frac{4}{5} V$$

$$V_{01} = \frac{1}{\pi} (\frac{6}{5}+j\frac{8}{5}) V$$

$$V_{01}(t) = \frac{1}{\pi} (\frac{6}{5}) \cos(w_0 t) - \frac{1}{\pi} (\frac{8}{5}) \sin(w_0 t) V$$
or  $V_{01}(t) = 0.382 \cos(3.2kt)$ 

$$= 0.510 \sin(3.2kt) V$$