
Fourier Series Circuit response Ex 3

Ex:

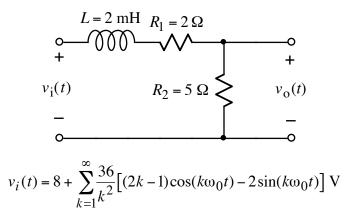

Write the time-domain expression of the sixth harmonic (i.e., k = 6) of  $v_0(t)$ .

**Note:**  $\omega_0 = 2 \text{ k rad/s for the Fourier series.}$ 

SOL'N: The sixth harmonic of  $v_0(t)$  arises solely from the sixth harmonic of  $v_{\overline{i}}(t)$  owing to the property of sinusoidal inputs producing only sinusoidal signals of the same freq guency everywhere in the circuit. Thus, we focus on  $v_{\overline{i}6}(t)$ :

$$v_{i6}(t) = \frac{36}{6^2} \left[ (2(6)-1) \cos(6w_0 t) - 2\sin(6w_0 t) \right] v$$
  

$$v_{i6}(t) = 11 \cos(12k_{1/3} \cdot t) - 2 \sin(12k_{1/3} t) v$$

We find the output  $v_{06}(t)$  for the circuit when  $v_{16}(t)$  is the input. The phasor of the input signal is

$$V_{i6} = 11 + j2.$$

We have a V-divider:

$$V_{06} = V_{16} \cdot \frac{R_2}{R_1 + R_2 + j \omega L}$$
 where  $\omega = 6 \omega_0$ 

or  $V_{06} = H(j 6 \omega_0) \overline{V}_{i6}$  where  $H(j 6 \omega_0) = \frac{R_2}{R_1 + R_2 + j 6 \omega_0 L}$ 

The impedance of L is

$$jwL = jGw_0L = jG\cdot 2kr/s\cdot 2mH = j24_R$$

Our transfer function is

$$H(j_{b}w_{o}) = 5 \mathcal{R} = 5$$
  
 $2\mathcal{R} + 5\mathcal{R} + j^{2} + \mathcal{R} = 7 + j^{2} + j^{2}$ 

combining results yields the value of Vos:

$$V_{06} = H(j_{6}\omega_{0})V_{16} = \frac{5}{7+j_{24}}(11+j_{2})V_{16}$$

To simplify this complex value, we rationalize:

$$V_{06} = \frac{5(11+j^2)}{7+j^24} \cdot \frac{7-j^{24}}{7-j^{24}} = \frac{5[(77+48)-j(254-14)]}{7^2+24^2} v$$
  
or  
$$V_{06} = \frac{5(125-j^250)}{7^2+250} v$$

$$V_{06} = \frac{5(125 - j250)}{25^2} v$$
  
or  
$$V_{06} = 1 - j2 v$$

Converting back to the time domain (and remembering that the inverse phasor of -j is sin(wt), we have the time domain expression for the sixth harmonic of vo(t):

$$v_{06}(t) = \cos(12kr/s \cdot t) + 2\sin(12kr/s \cdot t) V$$