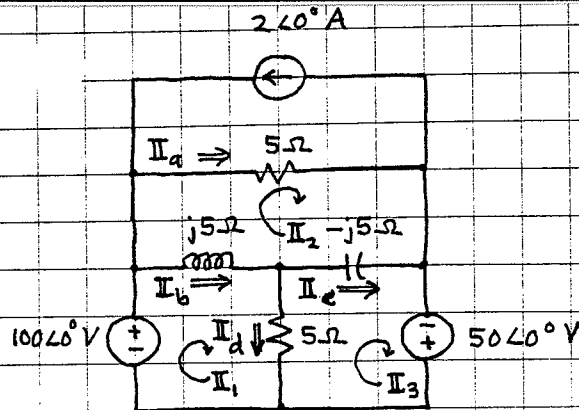


ex:



Use mesh-current method to find I_a, I_b, I_c, I_d .

sol'n: Define mesh currents (phasors) as indicated on above diagram. Note that the top loop lacks a mesh current because that loop must have current phasor equal to the $2\angle 0^\circ A$ of the current source on the outside edge of the loop. Note also that we could choose any mesh loop to be I_1 . The solution manual chose the lower left loop to be I_1 .

Now we write equations as we would for a DC circuit, but we use complex impedances instead of R 's and phasor current and voltage sources instead of real-valued current and voltage sources.

$$\text{Loop 1: } 100\angle 0^\circ V - I_1 j5\Omega - I_1 5\Omega = 0V \\ + I_2(j5\Omega) + I_3 5\Omega$$

$$\text{Loop 2: } -\cancel{I_2 j5\Omega} - I_2 5\Omega - \cancel{I_2(-j5\Omega)} = 0V \\ + I_1 j5\Omega - 2\angle 0^\circ A \cdot 5\Omega + I_3(-j5\Omega)$$

$$\text{Loop 3: } 50\angle 0^\circ V - I_3 5\Omega - I_3(-j5\Omega) = 0V \\ + I_1 5\Omega + I_2(-j5\Omega)$$

Now simplify. Put constants on right sides of eq'ns, and write left sides as:

$$I_1 \cdot \text{coeff} + I_2 \cdot \text{coeff} + I_3 \cdot \text{coeff}$$

$$\text{Loop 1: } I_1(5+j5)\Omega - I_2 j5\Omega + I_3(-5)\Omega = 100\angle 0^\circ \text{ V}$$

$$\text{Loop 2: } I_1(-j5)\Omega + I_2 5\Omega + I_3 j5\Omega = -2\angle 0^\circ \text{ A} \cdot 5\Omega = -10\angle 0^\circ \text{ V}$$

$$\text{Loop 3: } I_1(-5)\Omega + I_2 j5\Omega + I_3(5-j5)\Omega = 50\angle 0^\circ \text{ V}$$

Eliminate I_3 : eqn 1 + eqn 2 + eqn 3 =
(and by good fortune I_1 , too)

$$I_1(5+j5-j5-5)\Omega + I_2(-j5+5+j5)\Omega + I_3(-5+j5+5-j5)\Omega = 100\angle 0^\circ - 10\angle 0^\circ + 50\angle 0^\circ \text{ V}$$

$$I_2 = \frac{140\angle 0^\circ \text{ V}}{5\Omega} = 28 \text{ A}$$

Now solve for I_1 : j eqn 1 + eqn 2 =

$$I_1(-5+j5-j5)\Omega + I_2(5+5)\Omega + I_3(j5+j5)\Omega = \overset{5\angle 100^\circ}{j100\angle 0^\circ} - \overset{5\angle -10^\circ}{10\angle 0^\circ} \text{ V}$$

$$\text{or } I_1(-5)\Omega + 28\text{A} \cdot 10\Omega = -10 + j100 \text{ V}$$

$$\text{or } I_1(-5)\Omega = -290 + j100 \text{ V}$$

$$\text{or } I_1 = 58 - j20 \text{ A}$$

Now find I_3 from eqn 2:

$$(58-j20)\text{A}(-j5)\Omega + 28\text{A} \cdot 5\Omega + I_3 j5\Omega = -10 \text{ V}$$

$$\text{or } I_3 = \frac{-10 + 100 + j290 + -140 \text{ V}}{j5\Omega} = 58 + j10 \text{ A}$$

$$I_a = I_2 + 2\angle 0^\circ \text{ A} = 28\text{A} + 2\text{A} = 30\text{A} \quad I_b = I_1 - I_2 = 58 - j20 - 28\text{A} = 30 - j20\text{A}$$

$$I_c = I_3 - I_2 = 58 + j10 - 28\text{A} = 30 + j10\text{A} \quad I_d = I_1 - I_3 = 58 - j20 - 58 - j10\text{A} = -j30\text{A}$$