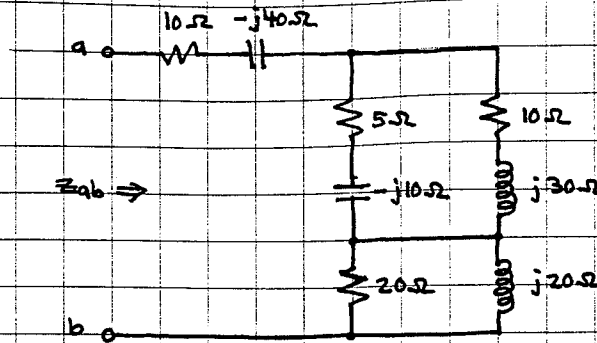


ex:



Find impedance Z_{ab} .

sol'n: Use same formulas for series and parallel z 's as you would for R 's.

$$Z_{ab} = 10\Omega + -j40\Omega + (5\Omega - j10\Omega) \parallel (10\Omega + j30\Omega) + 20\Omega \parallel j20\Omega$$

Consider parallel z pieces:

$$\begin{aligned} 20\Omega \parallel j20\Omega &= 20\Omega \cdot \parallel j = 20\Omega \cdot \frac{1 \cdot j}{1+j} \\ &= 20\Omega \left(\frac{j}{1+j} \cdot \frac{1-j}{1-j} = \frac{1+j}{1^2+1^2} = \frac{1}{2} + j\frac{1}{2} \right) \\ &= 10\Omega + j10\Omega \end{aligned}$$

$$\begin{aligned} (5\Omega - j10\Omega) \parallel (10\Omega + j30\Omega) &= 5\Omega \cdot (1-j2) \parallel (2+j6) \\ &= 5\Omega \cdot \frac{(1-j2)(2+j6)}{1-j2+2+j6} = 5\Omega \cdot \frac{2+12+j(6-4)}{3+j4} \\ &= 5\Omega \cdot \frac{14+j2}{3+j4} \cdot \frac{3-j4}{3-j4} = 5\Omega \cdot \frac{42+8+j(6-56)}{3^2+4^2} \\ &= 5\Omega \cdot \frac{50-j50}{25} = 5\Omega \cdot (2-j2) \\ &= 10\Omega - j10\Omega \end{aligned}$$

$$\begin{aligned} Z_{ab} &= 10\Omega - j40\Omega + 10\Omega + j10\Omega + 10\Omega - j10\Omega \\ &= 30\Omega - j40\Omega \end{aligned}$$

polar form: $Z_{ab} = \sqrt{30^2+40^2} e^{j \tan^{-1} \frac{-40}{30}} = 50 e^{-j53^\circ} \Omega$