

TOOL: Once a parallel impedance is simplified to a single (real) resistance in parallel with a single imaginary impedance, (1) and (2) give the value of the equivalent impedance.

$$R||jX = \frac{RX}{R^2 + X^2}(X + jR) \quad \text{Rectangular form} \quad (1)$$

$$R||jX = \frac{RX}{\sqrt{R^2 + X^2}} e^{j \tan^{-1}(R/X)} \quad \text{Polar form} \quad (2)$$

DERIV: Derivation of formulas (1) and (2).

$$R||jX = \frac{jRX}{R + jX} \cdot \frac{R - jX}{R - jX}$$

$$R||jX = \frac{RX^2}{R^2 + X^2} + j \frac{R^2X}{R^2 + X^2}$$

$$R||jX = \frac{RX}{R^2 + X^2} \cdot (X + jR) \quad \text{Rect} \quad (1)$$

$$R||jX = \frac{RX}{R^2 + X^2} \cdot \sqrt{R^2 + X^2} e^{j \tan^{-1}(R/X)}$$

$$R||jX = \frac{RX}{\sqrt{R^2 + X^2}} e^{j \tan^{-1}(R/X)} \quad \text{Polar} \quad (2)$$