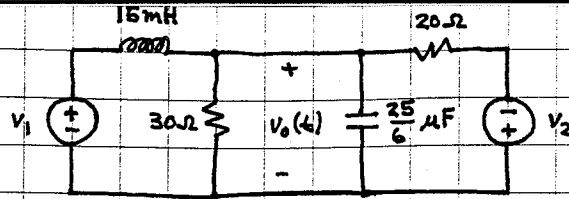


ex:



$$v_1(t) = 240 \cos(4000t + 53.13^\circ) \text{ V}$$

$$v_2(t) = 96 \sin(4000t) \text{ V}$$

Use source transformations to find steady-state $v_0(t)$.

sol'n: Find Norton equivalents for left and right sides.

(Note: One could also use Thevenin equivalents.)

First, convert sources to phasors:


$$V_1 = 240 \angle 53.13^\circ \text{ V} \quad \text{Note: } \omega = 4000 \text{ from } 4000t + \dots$$

$$V_2 = 96 \angle -90^\circ \text{ V} \quad \text{since } \sin(\omega t) = \cos(\omega t - 90^\circ)$$

Second, convert L's and C's to impedances:

$$z_L = j\omega L = j4000 \cdot 15\text{m} = j60 \Omega$$

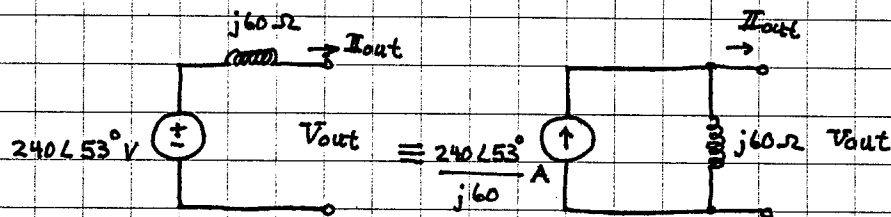
$$z_C = \frac{-j}{\omega C} = \frac{-j}{4000 \cdot \frac{25}{6} \mu} = \frac{-j6}{100\text{k} \cdot \mu} = -j60 \Omega$$



Make open-circuit V_{out} 's match, and make short-circuit I_{out} 's match. Result corresponds to case


of DC v -source and R , but current source is

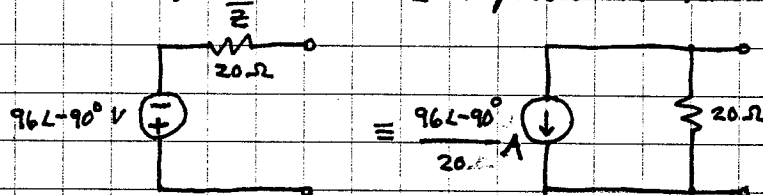now $\frac{V}{z}$ and z replaces R across source.



New circuit with Norton equivalents:
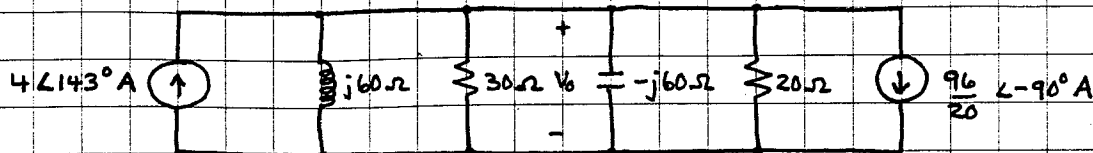
$$240 \angle 53^\circ / j60 = 240 \angle 53^\circ / 60 e^{+j90^\circ} = \frac{240}{60} \angle 53^\circ - 90^\circ$$



$$\text{Phasor } V_o = \left(4 \angle -37^\circ - \frac{96}{20} \angle -90^\circ \right) A \cdot j60 \parallel 30 \parallel -j60 \parallel 20 \Omega$$

$$4 \angle -37^\circ = +3.19 - j2.41 \quad \frac{96}{20} \angle -90^\circ = -j4.8$$

(Recall that $Re^{j\theta}$ or $R \angle \theta = R \cos \theta + jR \sin \theta$.)


$$4 \angle -37^\circ - \frac{96}{20} \angle -90^\circ = +3.19 - j2.41 - -j4.8 = 3.19 + j2.39$$

$$\approx 3.2 + j2.4$$

$$\text{Use } \frac{1}{Z_{\text{Tot}}} = \frac{1}{j60 \Omega} + \frac{1}{30 \Omega} + \frac{1}{-j60 \Omega} + \frac{1}{20 \Omega}$$

$$\text{or } Z_{\text{Tot}} = 30 \parallel 20 \Omega = 10 \Omega \cdot \frac{3}{2} = 10 \Omega \cdot \frac{3.2}{3+2} = 12 \Omega$$

Simplified circuit:

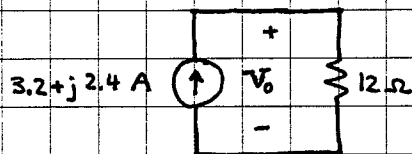

$$\begin{aligned} V_o &= (3.2 + j2.4 A) \cdot 12 \Omega \\ &= 38.4 + j28.8 V \\ &= \left(\sqrt{3.2^2 + 2.4^2} \angle \tan^{-1} \frac{2.4}{3.2} \right) \cdot 12 \end{aligned}$$

$$V_o = 48 \angle 37^\circ V$$

$$\therefore v_o(t) = 48 \cos(4000t + 37^\circ) V$$