

Find Thevenin equivalent circuit with respect to a-b.

sol'n: Find V_{TH} as open circuit output V_0 .
Find Z_{TH} by turning independent sources to zero and connecting $120^\circ V$ source to output.
Then $Z_{TH} = \frac{120^\circ V}{I_0}$

$$V_{TH} = \frac{V_1}{-j150\Omega + 40\Omega} - 0.02 V_0 + \frac{V_1 - 75\angle 0^\circ V}{600\Omega + j150\Omega} = 0A$$

$$V_0 = V_1 \frac{40\Omega}{-j150\Omega + 40\Omega}$$

$$V_1 \left(\frac{1}{-j150\Omega + 40\Omega} - \frac{0.02}{-j150\Omega + 40\Omega} + \frac{1}{600\Omega + j150\Omega} \right) = 0$$

$$= \frac{75\angle 0^\circ V}{600\Omega + j150\Omega}$$

$$V_1 \left(0.2 + \frac{40\Omega - j150\Omega}{600\Omega + j150\Omega} \right) = \frac{75 V (40\Omega - j150\Omega)}{600\Omega + j150\Omega}$$

$$V_1 (120\Omega + j30\Omega + 40\Omega - j150\Omega) = 75 V (40\Omega - j150\Omega)$$

$$V_1 = \frac{75 V (4 - j15)}{16 - j12} = \frac{75 V (4 - j15)}{4 (4 - j3)} = \frac{75 V \sqrt{16+225} \tan^{-1} \frac{-15}{4}}{4 \cdot 5\Omega e^{j \tan^{-1} \frac{-3}{4}}}$$

$$= 58.2 V e^{j(\tan^{-1} \frac{3}{4} + \tan^{-1} \frac{-15}{4})}$$

$$= 58.2 \angle \left(\tan^{-1} \frac{3}{4} + \tan^{-1} \frac{-15}{4} \right)$$

$$V_o = \frac{40 \Omega}{40 \Omega - j150 \Omega} V_1$$

$$= \frac{4}{4 - j15} V_1$$

$$= \frac{4.75 \text{ V}}{20 e^{j \tan^{-1} \frac{3}{4}}}$$


$$= 15 \angle \tan^{-1} \frac{3}{4} \text{ V}$$

$$V_{Th} = V_o = 15 \angle 36.9^\circ \text{ V}$$

$$Z_{Th} = \frac{1 \angle 0^\circ \text{ V}}{I_a}$$

Connect 1V source (sinusoidal) to a-b.
Turn independent source to 0.

$$V_o = 1 \angle 0^\circ \text{ V}$$

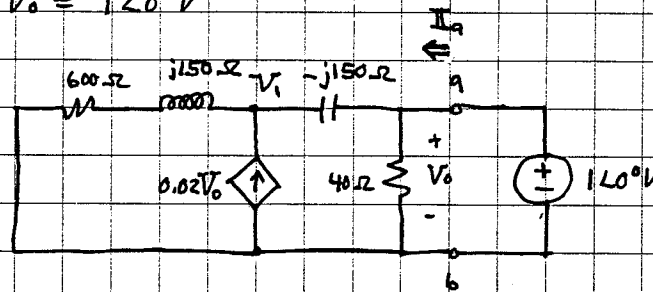

Use Node-v to find V_1 . $0.02V_o = 0.02 \cdot 1 \angle 0^\circ = 0.02 \text{ A}$.

$$\frac{V_1}{600 \Omega + j150 \Omega} - 0.02 \text{ A} + \frac{V_1 - 1 \angle 0^\circ \text{ V}}{-j150 \Omega} = 0 \text{ A}$$

$$V_1 \left(\frac{1}{600 \Omega + j150 \Omega} + \frac{1}{-j150 \Omega} \right) = \frac{1 \angle 0^\circ \text{ V}}{-j150 \Omega} + 0.02 \text{ A}$$

$$V_1 \left(1 + \frac{600 \Omega + j150 \Omega}{-j150 \Omega} \right) = \left(\frac{1 \text{ V}}{-j150 \Omega} + 0.02 \text{ A} \right) (600 \Omega + j150 \Omega)$$

$$V_1 (-j150 \Omega + 600 \Omega + j150 \Omega) = (+1 \text{ V} - \overbrace{j0.02 \cdot 150 \text{ V}}^{j3}) (600 \Omega + j150 \Omega)$$

$$V_1 = (+1 - j3) (600 \Omega + j150 \Omega) / 600 \Omega$$

$$V_1 = (1 - j3) \left(1 + \frac{j}{4} \right) = 1 + \frac{3}{4} + j \left(\frac{1}{4} - 3 \right) = \frac{7}{4} - j \frac{11}{4}$$

$$-I_a = \frac{V_1 - 1 \angle 0^\circ \text{ V}}{-j150 \Omega} - \frac{1 \angle 0^\circ \text{ V}}{40 \Omega}$$

$$= \frac{1}{10} \left(\frac{jV_1 - j}{15} - \frac{1}{4} \right)$$

$$= \frac{1}{10} \frac{1}{60} (j4V_1 - j4 - 15)$$

$$= \frac{1}{600} (j(7 - j11) - j4 - 15)$$

$$= \frac{1}{600} (j3 - 4)$$

$$Z_{TH} = \frac{1 \angle 0^\circ \text{ V}}{I_a}$$

$$= \frac{-600}{j3 - 4} \Omega$$

$$= \frac{-600}{3^2 + 4^2} (-j3 - 4)$$

$$= + \frac{600}{25} (4 + j3)$$

$$= + 24 (4 + j3)$$

$$= + 24 \sqrt{4^2 + 3^2} e^{j \tan^{-1} \frac{3}{4}}$$

$$= + 120 e^{j 36.87^\circ}$$