

TOOL: By shifting time t , the phase shift of an AC current waveform may be set to zero, and the phase shift of the AC voltage waveform may be written as the difference, ϕ_{v-i} , between the voltage phase shift and the current phase shift:

$$i(t) = I_m \cos(\omega t), \text{ and}$$

$$v(t) = V_m \cos(\omega t + \phi_{v-i}).$$

The power waveform may then be written as follows:

$$p(t) = \mathbf{P} + \mathbf{P} \cos(2\omega t) - \mathbf{Q} \sin(2\omega t)$$

where

$$\mathbf{P} = \frac{V_m I_m}{2} \cos(\phi_{v-i}) \text{ and}$$

$$\mathbf{Q} = \frac{V_m I_m}{2} \sin(\phi_{v-i})$$

TOOL: The phasor for the AC power waveform, is known as complex power, \mathbf{S} , and while \mathbf{S} technically describes only the sinusoidal part of the waveform, the real part of \mathbf{S} is equal to the Average Power (a.k.a. DC power), \mathbf{P} :

$$\mathbf{S} = \mathbf{P} + j\mathbf{Q}$$

Thus, the complex power (phasor) contains all the information about the power.

DEF: $\mathbf{P} \equiv$ Average Power \equiv DC power \equiv Active power \equiv Real power, units = Watts (W)

DEF: $\mathbf{Q} \equiv$ Reactive Power, units volt-amps reactive = (VAR)

DEF: $\mathbf{S} \equiv$ Complex Power, units volt-amps = (VA)

DEF: $|\mathbf{S}| \equiv$ Apparent Power = $\sqrt{\mathbf{P}^2 + \mathbf{Q}^2}$, units = (VA)

DEF: Power Factor $\equiv \cos(\theta_{v-i}) = \mathbf{P}/\mathbf{S}$, unitless

NOTE: All power units are equivalent to Watts, but distinct letters are used so that power terms for \mathbf{P} , \mathbf{Q} , and \mathbf{S} , may be distinguished from one another by the units when they are written as numbers. (Note that \mathbf{S} may lack an imaginary part.)


TOOL: Complex power, \mathbf{S} , may be computed using the following formulas involving phasors \mathbf{I} and \mathbf{V} for current and voltage, and/or impedance Z :

$$\mathbf{S} = \frac{1}{2} \mathbf{V} \mathbf{I}^* = \frac{|\mathbf{I}|^2 Z}{2} = \frac{|\mathbf{V}|^2}{2Z^*} = |\mathbf{I}_{\text{rms}}|^2 Z = \frac{|\mathbf{V}_{\text{rms}}|^2}{Z^*}$$

where $*$ \equiv conjugate (change all j 's to $-j$'s), $\mathbf{I} = I_m \angle 0^\circ$, $\mathbf{V} = V_m \angle \phi_{v-i}$,

and rms \equiv root-mean-square = $\sqrt{\frac{1}{T} \int_{t=0}^T f^2(t) dt}$ where T is one period of waveform.

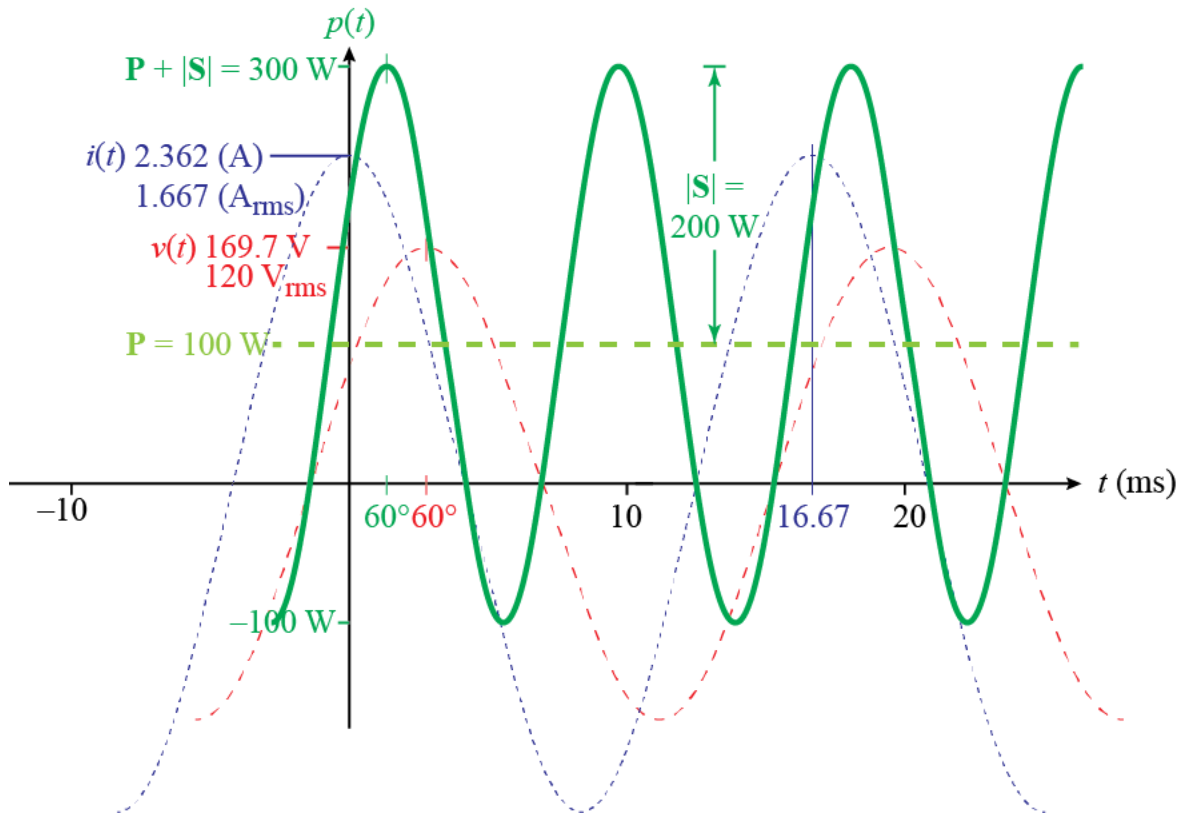TOOL: The figure below shows the AC waveforms for v , i , and p with variables related to complex power indicated. 100 W average power, 120 VAC at 60 Hz.



time-domain waveform

$$i(t) = 2.362 \cos(\omega t) \text{ A}$$

$$v(t) = 169.7 \cos(\omega t - 60^\circ) \text{ V}$$

$$p(t) = \mathbf{P} + \mathbf{P} \cos(2\omega t) - \mathbf{Q} \sin(2\omega t)$$

phasor

$$\mathbf{I} = 2.362 \angle 0^\circ \text{ A}$$

$$\mathbf{V} = 169.7 \angle -60^\circ \text{ V}$$

$$\mathbf{S} = \mathbf{P} + j\mathbf{Q} = \frac{|\mathbf{V}||\mathbf{I}|}{2} \cos(-60^\circ) \text{ W} + j \frac{|\mathbf{V}||\mathbf{I}|}{2} \sin(-60^\circ) \text{ VAR}$$