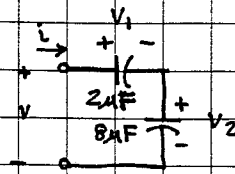


ex:




$$i = 240e^{-10t} \mu\text{A} \quad t \geq 0$$

$$v_1(t=0) = -10\text{V} \quad v_2(t=0) = -5\text{V}$$

Calculate total energy trapped in C's as $t \rightarrow \infty$.
Hint: Don't combine C's in series - find energy for each C and sum them.

Note: The energy trapped in C's refers to energy that we cannot extract from the C's when the total v across the two C's in series is 0V.

For example:

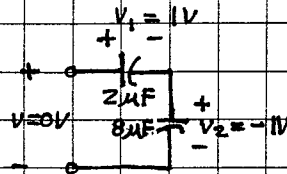

Here we have
 $v_1 + v_2 = v = 0\text{V}$,
but each C has
 $v \neq 0$ across it.

If we connect an R across the terminals, we will get no current flow because $v = 0\text{V}$. Thus, we cannot access the "trapped" energy.

$$\text{The trapped energy is } w_{C1} + w_{C2} = \frac{1}{2} 2\mu\text{F} (+1\text{V})^2 + \frac{1}{2} 8\mu\text{F} (-1\text{V})^2$$

$$= 1\mu\text{J} + 4\mu\text{J} = 5\mu\text{J}.$$


(Note that for series combination we would get $\frac{1}{2} C_{eq} v^2 = \frac{1}{2} C_{eq} \cdot 0\text{V}^2 = 0\text{J}$.)

Note: The energy stored in C's refers to energy that we can extract from the C's by connecting a circuit to the two terminals having series C's between.

For the stored energy, we get the correct answer if we use $C_{eq} = C_1 \parallel C_2 = \frac{C_1 C_2}{C_1 + C_2}$, (see next page).

moral: We can use C_{eq} if all we care about are the i and v at terminals, (or the energy we can extract from the terminals).

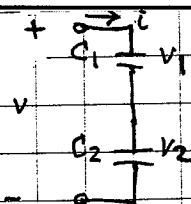We now consider this energy issue in detail before finally solving the problem.



Assume no energy is trapped when $v=0$.

Now let current i flow until time t .

$$i = C \frac{dv}{dt} \Rightarrow \int i dt = C_i v_i \text{ for each } C_i = C_1 \text{ or } C_2.$$

Both C's see same i (since in series), so

$\int i dt$ same for both C_1 and C_2 .

$$\therefore C_1 v_1 = C_2 v_2 \quad \text{or} \quad v_2 = \frac{C_1}{C_2} v_1$$

$$\text{Now, } C_{eq} = C_1 \parallel C_2 = \frac{C_1 C_2}{C_1 + C_2}$$

$$\begin{aligned} \frac{1}{2} C_{eq} v^2 &= \frac{1}{2} C_{eq} (v_1 + v_2)^2 = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} \left(v_1 + \frac{C_1}{C_2} v_1 \right)^2 \\ &= \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} \left[\frac{(C_1 + C_2) v_1}{C_2} \right]^2 \\ &= \frac{1}{2} \frac{C_1}{C_2} (C_1 + C_2) v_1^2 \end{aligned}$$

$$\begin{aligned} \frac{1}{2} C_1 v_1^2 + \frac{1}{2} C_2 v_2^2 &= \frac{1}{2} C_1 v_1^2 + \frac{1}{2} C_2 \left(\frac{C_1}{C_2} v_1 \right)^2 \\ &= \frac{1}{2} \left(C_1 + \frac{C_1^2}{C_2} \right) v_1^2 \\ &= \frac{1}{2} \frac{C_1}{C_2} (C_1 + C_2) v_1^2 \\ &= \frac{1}{2} C_{eq} v^2 \quad \checkmark \end{aligned}$$

If there is trapped energy, then when $v \neq 0$ we have $v_1 = v_0$ and $v_2 = -v_0$ for some voltage v_0 .

If we let current i flow and store energy then we have

$$\int i dt = C_1 (v_1 - v_0) = C_2 (v_2 + v_0), \text{ or } v_2 = \frac{1}{C_2} [C_1 v_1 - (C_1 + C_2) v_0]$$

The stored energy on C_{eq} is $\frac{1}{2} C_{eq} v^2 = \frac{1}{2} C_{eq} (v_1 + v_2)^2$

This is equal to the total energy for C_1 and C_2 minus the trapped energy. In other words the stored energy is

$$\underbrace{\frac{1}{2} C_1 v_1^2 + \frac{1}{2} C_2 v_2^2}_{\text{total energy}} - \underbrace{\left(\frac{1}{2} C_1 v_0^2 + \frac{1}{2} C_2 v_0^2 \right)}_{\text{trapped energy}} = \underbrace{\frac{1}{2} C_{eq} v^2}_{\text{stored energy}}$$

We now find $v_1(t \rightarrow \infty)$ and $v_2(t \rightarrow \infty)$.

$$i = 240 e^{-10t} \mu A = C_1 \frac{dv_1}{dt} = C_2 \frac{dv_2}{dt} \quad \text{same } i \text{ flows thru capacitors in series}$$

$$\int_{t=0}^{t=\infty} i(t) dt = \int_{t=0}^{t=\infty} 240 e^{-10t} \mu A dt = \int_{v_1(t=0)}^{v_1(t=\infty)} C_1 dv_1 = \int_{v_2(t=0)}^{v_2(t=\infty)} C_2 dv_2$$

$$\frac{240}{-10} e^{-10t} \mu A \Big|_{t=0}^{t=\infty} = C_1 [v_1(t=\infty) - v_1(t=0)] = C_2 [v_2(t=\infty) - v_2(t=0)]$$

$$-24 \mu A \Big|_{t=0}^{t=\infty} = 2 \mu F [v_1(t=\infty) - 10V] = 8 \mu F [v_2(t=\infty) - 5V]$$

$$24 \mu A \cdot s = 2 \mu F [v_1(t=\infty) + 10V] = 8 \mu F [v_2(t=\infty) + 5V]$$

$$v_1(t=\infty) = \frac{24 \mu A \cdot s}{2 \mu F} - 10V = 12V - 10V = 2V$$

$$v_2(t=\infty) = \frac{24 \mu A \cdot s}{8 \mu F} - 5V = 3V - 5V = -2V$$

$$\text{Energy trapped} \equiv W_{\text{trapped}} = \frac{1}{2} C_1 v_1^2(t=\infty) + \frac{1}{2} C_2 v_2^2(t=\infty)$$

$$= \frac{1}{2} 2 \mu F \cdot (2V)^2 + \frac{1}{2} 8 \mu F (-2V)^2$$

$$= 4 \mu J + 16 \mu J$$

$$= 20 \mu J$$

Note: The given $i = 240 e^{-10t}$ leaves us with $v = v_1(t=\infty) + v_2(t=\infty) = 0V$. We must have $v = 0V$ for the calculation of the trapped energy. Otherwise, we also have stored energy $= \frac{1}{2} C_{\text{eq}} v^2$.

A different i might not have resulted in $v = 0$ as $t \rightarrow \infty$.