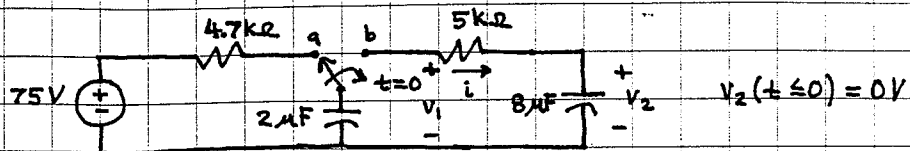


ex:




The switch in the circuit has been in position 'a' for a long time before it changes to position 'b' at $t=0$.

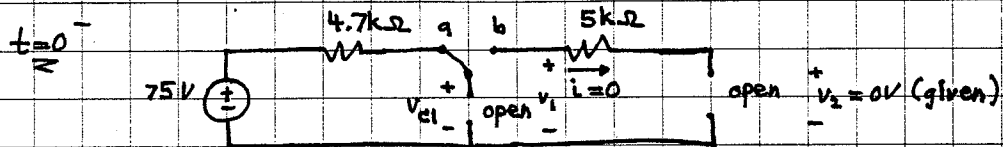a) Find i , v_1 , and v_2 for $t \geq 0^+$.


At $t=0^-$ we have $\frac{dv_1}{dt} = 0$ both C's.

$\therefore i_2 = 0$ for both C's. \therefore C's look like open circuits



Since no current flows on the left side, there is no V -drop across the $4.7k\Omega$ R. Thus, $v_{c1} = 75V$.

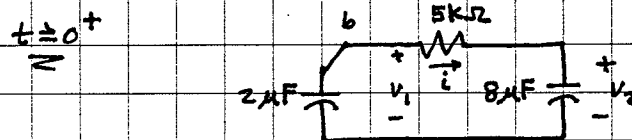When we throw the switch at $t=0$, the left side 75V and $4.7k\Omega$ no longer affect i , v_1 , and v_2 :




We combine the two C's in series into one $C_{eq} = 2\mu F // 8\mu F$;

$$C_{eq} = \frac{2\mu F \cdot 8\mu F}{2\mu F + 8\mu F} = \frac{16\mu F}{10} = 1.6\mu F.$$

The initial voltage on C_{eq} is $v_1(0^+) - v_2(0^+) = v_1(0^-) - v_2(0^-)$, since V across C's cannot change instantly.

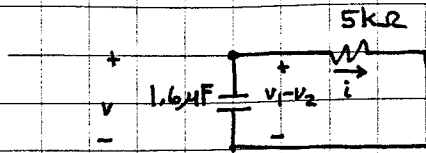Now our equivalent circuit is an RC with initial voltage $v_{c1} - v_{c2} = 75V - 0 = 75V$:



We sum currents flowing out of node between R & C, (instead of summing V's around loop as we did for RL problems).

In other words, we equate the i in the R & C.

$$-i = C \frac{d v_1 - v_2}{dt} \equiv C \frac{dV}{dt} \quad \text{and} \quad i = \frac{v_2 - v_1}{R} \equiv \frac{V}{R}$$

$$\therefore \frac{V}{R} = -C \frac{dV}{dt} \quad \text{or} \quad \frac{V}{R} + C \frac{dV}{dt} = 0A$$

As shown on p.287 of text, the solution is

$$v(t) = v(t=0^+) e^{-t/RC_{eq}} = 75V \cdot e^{-t/5k\Omega \cdot 1.6\mu F} = 75V \cdot e^{-t/8ms}$$

$$i(t) = \frac{v(t)}{R} = \frac{75V}{5k\Omega} e^{-t/8ms} = 15mA e^{-t/8ms}$$

Now that we have i(t), we can integrate i(t) to find v₁(t) and v₂(t).

$$-i(t) = C_1 \frac{d v_1}{dt}$$

$$-\int_{t=0^+}^{t'=t} i(t') dt' = C_1 \int_{v_1(t=0^+)}^{v_1(t)} d v_1$$

$$i(t) = C_2 \frac{d v_2}{dt}$$

$$\int_{t=0^+}^{t'=t} i(t') dt' = C_2 \int_{v_2(t=0^+)}^{v_2(t)} d v_2$$

$$60V \cdot \left(\frac{-8ms \cdot 15mA}{2\mu F} \right) e^{-t'/8ms} \Big|_{t'=0}^{t'=t} = v_1(t) - v_1(0^+)$$

$$\left(\frac{-8ms \cdot 15mA}{8\mu F} \right) e^{-t'/8ms} \Big|_{t'=0}^{t'=t} = v_2(t) - v_2(0^+)$$

$$v_1(t) = 60V \left(e^{-t/8ms} - 1 \right) + 75V$$

$$v_2(t) = -15V \left(e^{-t/8ms} - 1 \right)$$