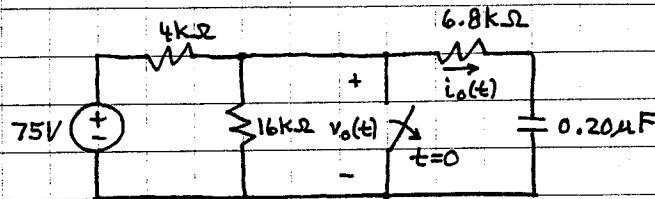



ex:



Switch has been closed for a long time before opening at time $t=0$.

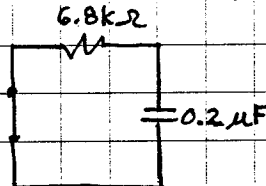a) Find initial value of $i_o(t)$.

sol'n: If switch was closed for a long time, then the capacitor will discharge through $6.8k\Omega$:




(Right side of circuit, see 'note' below.)

Note: The closed switch creates a short circuit. The left and right sides of the circuit may then be treated as though they are totally independent. Why? Because the currents flowing through the short create ^{two} no V drop. Thus, the mesh currents on the ^{two} sides of the short do not interact.

Thus, at $t=0^-$ the C has no charge, and $v_c = 0$.
 $\therefore C$ acts like short at $t=0^-$. Since v_c cannot change instantly, $v_c(t=0^+) = 0V$, too.

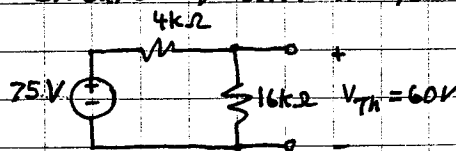
Also, we replace the $75V$ and $4k\Omega$ and $16k\Omega$ with a Thevenin equivalent. V_{TH} from open-circuit V -divider is $75V \cdot \frac{16k\Omega}{4k\Omega + 16k\Omega} = 60V = V_{TH}$



Turn $75V$ down to $0V$ and connect $1V$ source to output to get $R_{TH} = 1V / [1V / (4k\Omega \parallel 16k\Omega)] = 4k\Omega \parallel 16k\Omega$

$$R_{TH} = 4k\Omega \cdot 1/4 = 4k\Omega \cdot \frac{4}{5} = 3.2k\Omega$$

\therefore Circuit model for $t=0^+$ is:

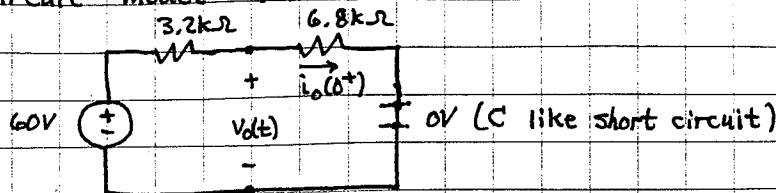

$$i_o(t=0^+) = \frac{60V}{3.2k\Omega + 6.8k\Omega} = \frac{60V}{10k\Omega} = \frac{6V}{1k\Omega} = 6mA$$

b) Find $i_o(t \rightarrow \infty)$.

sol'n: When the C is charged, it looks like open circuit.

Note: $i_o(t \rightarrow \infty) = 0A$ for all C's in all switching probs.

$v_c(t=0^-) = v_c(t=0^+)$ " " " " " " " "

But $v_c(t=0^-) = 0V$ only if circuit discharges C completely for $t < 0$. Otherwise, $v_c(t=0^-)$ is some nonzero value.

If C is open circuit, then $i_o(t \rightarrow \infty) = 0A$.

c) Find time constant for $t \geq 0$.

$$\begin{aligned} \text{sol'n: } \tau &= R_{eq} \cdot C & R_{eq} &= 10k\Omega = 3.2k\Omega + 6.8k\Omega \\ &= 10k\Omega \cdot 0.2\mu F & C &= 0.2\mu F \\ &= 2ms \end{aligned}$$

d) Find expression for $i_o(t)$ when $t \geq 0^+$

sol'n: General sol'n for $i_o(t)$ is:

$$\begin{aligned} i_o(t) &= i_o(t=0^+) + [i_o(t \rightarrow \infty) - i_o(t=0^+)] [1 - e^{-t/RC}] \\ &= 6mA + [0 - 6mA] [1 - e^{-t/2ms}] \\ &= 6mA e^{-t/2ms} \quad t \geq 0^+ \end{aligned}$$

e) Find expression for $v_o(t)$ when $t \geq 0^+$.

$$\begin{aligned} \text{sol'n: } v_o(t) &= 60V - i_o(t) \cdot 3.2k\Omega = 60V - 6mA \cdot e^{-t/2ms} \cdot 3.2k\Omega \\ &= 60V - 19.2V e^{-t/2ms} \quad t \geq 0^+ \end{aligned}$$