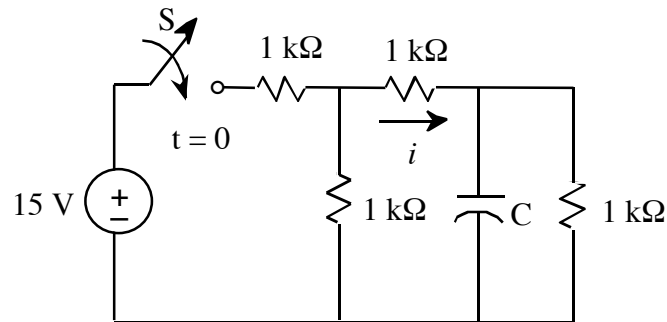


**EX:** In the circuit below, based on the interpretation that an uncharged capacitance initially looks like a short circuit and finally like an open circuit, give a qualitative description of the current  $i$  over time.



**ANS:** When the switch is first closed,  $C$  looks like a short circuit. Hence at  $t = 0^+$ ,  $i$  can be found from voltage division to be 5 mA. As  $t \rightarrow \infty$ ,  $C$  begins to look like an open circuit, in which case  $i$  can again be found from current division to be  $i = 3$  mA. Thus the asymptotic value of  $i$  is 3 mA. Consequently,  $i$  decreases smoothly from an initial value of 5 mA to a final value of 3 mA at a rate that depends on the time constant,  $R_t C_2$ , where  $R_t$  is the Thevenin equivalent resistance across  $C$ . For a small value of  $C$ , the decay will be fast; for a larger value of  $C$ , the decay will be slower.