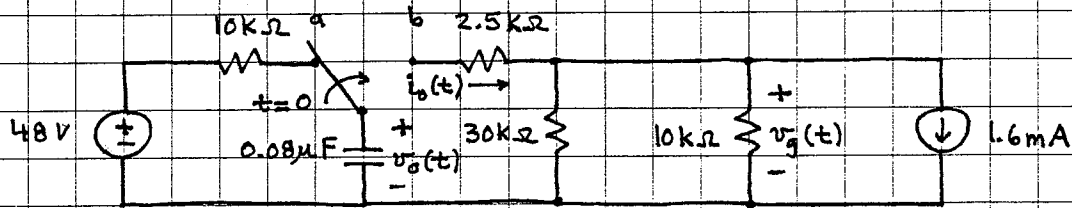


ex:



Find a)  $v_o(t \geq 0)$  b)  $i_o(t \geq 0)$  c)  $v_g(t \geq 0)$  d)  $v_g(0^+)$

ans: a)  $v_o(t \geq 0) = -12 + 60 e^{-t/0.8ms}$  V

b)  $i_o(t \geq 0) = 6 e^{-t/0.8ms}$  mA

c)  $v_g(t \geq 0) = -12 + 45 e^{-t/0.8ms}$  V


d)  $v_g(0^+) = 33V$

sol'n: a) Step 1: Find  $v$ 's for capacitors for  $t=0^-$   
 "  $i$ 's " inductors " "

(Here, we just have one C.)

tool:  $i$  (for C) = 0 at  $t=0^-$  open circuit  
 $v$  (" L) = 0 " " wire

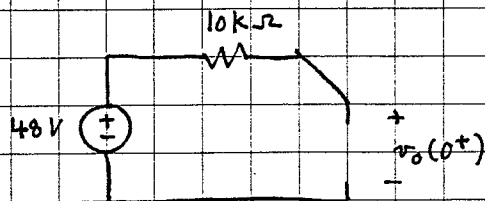$t=0^-$  circuit: (can ignore right side of circuit)




Since no current flows,  
 $V$  drop across  $10k\Omega = 0V$ .

$\therefore v_o(0^+) = 48V$

Step 2:  $v$  on C cannot change instantly  
 " " L " " "

Use  $\uparrow$  to find  $v$ 's and  $i$ 's at  $t=0^+$

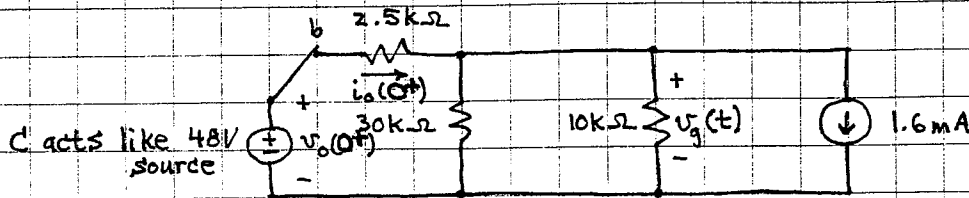$t=0^+$  circuit: (can ignore left side of circuit)



Note: At  $t=0^+$  we model C as V source  
 " " " " L " i source

Clearly,  $v_o(0^+) = 48V$ .

We use node voltage method to find  $v_g(t)$ .

$$\frac{v_g - 48V}{2.5k\Omega} + \frac{v_g}{30k\Omega} + \frac{v_g}{10k\Omega} + 1.6mA = 0A$$

$$\left( \text{or } \frac{v_g}{2.5k\Omega \parallel 30k\Omega \parallel 10k\Omega} = \frac{48V - 1.6mA}{2.5k\Omega} \right)$$

mult by 30k $\Omega$  both sides or  $(v_g - 48V)12 + v_g + 3v_g + 1.6mA(30k\Omega) = 0$

or  $16v_g = 48V \cdot 12 - 1.6(30)V = 48V \cdot 12 - 16(3)V$


or  $v_g = 3 \cdot 12 - 3 = 33V$

Thus,  $v_g(t=0^+) = 33V$  (answer to "d")

So  $i_o(t=0^+) = \frac{48V - 33V}{2.5k\Omega} = \frac{15V}{2.5k\Omega} = 6mA$

Step 3: Find v's for capacitors for  $t \rightarrow \infty$   
 " i's " inductors " "

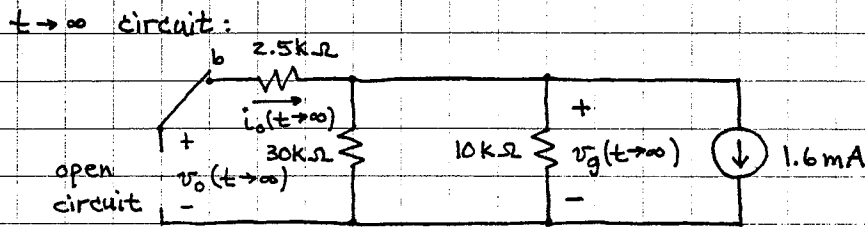Use these to find other i's and v's in circuit.  
 use tool:  $i(\text{for } C) = 0$  and  $v(\text{for } L) = 0$  at  $t \rightarrow \infty$



$$i_o(t \rightarrow \infty) = 0 \quad \text{since } C \text{ is open circuit}$$

Since  $i_o(t \rightarrow \infty) = 0$ , we have no V-drop across  $2.5k\Omega$  resistor.

$$\therefore v_o(t \rightarrow \infty) = v_g(t \rightarrow \infty)$$

To find  $v_g(t \rightarrow \infty)$  we observe that we have current divider consisting of the  $30k\Omega$  and  $10k\Omega$  resistors. The voltage,  $v_g(t \rightarrow \infty)$ , will be given by  $-1.6mA \cdot 10k\Omega \parallel 30k\Omega$ .

$$v_g(t \rightarrow \infty) = -1.6mA \cdot 10k\Omega \cdot \frac{1}{1+3} = -16V \cdot \frac{3}{4} = -12V$$


Step 4: Take Thevenin equivalent of circuit without C or without L.  $R_{Th}$  is R value for time constant.

Combine series or parallel C's or L's to obtain equivalent  $C_{eq}$  or  $L_{eq}$  for time constant.



For RC circuit, time constant =  $R_{Th} C_{eq}$

For RL circuit, " " =  $L_{eq} / R_{Th}$

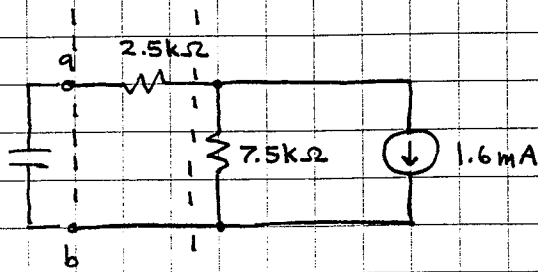Here, we have  $10k\Omega \parallel 30k\Omega = 10k\Omega \cdot \frac{1}{1+3} = 2.5k\Omega$  as resistance across  $1.6mA$ .



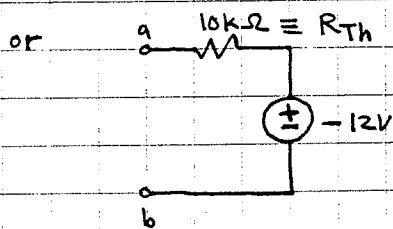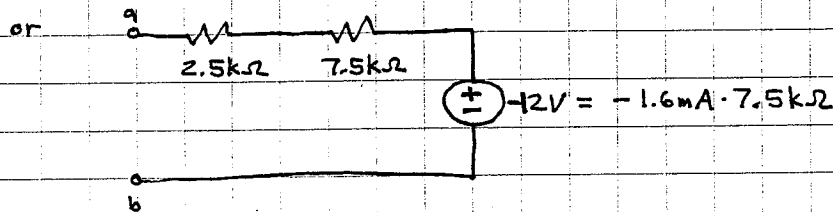Thev equiv  $\Rightarrow$   
Take Thev equiv  $\Rightarrow$   
and add  $2.5k\Omega$



$$\text{Time constant} = R_{Th} \cdot C = 10k\Omega \cdot 0.08\mu F = 0.8 \text{ ms}$$

Step 5: Use general form of sol'n for all  $i$ 's and  $v$ 's in the circuit:

$$i(t \geq 0) = i(t \rightarrow \infty) + [i(0^+) - i(t \rightarrow \infty)] e^{-t/\tau}$$

$$v(t \geq 0) = v(t \rightarrow \infty) + [v(0^+) - v(t \rightarrow \infty)] e^{-t/\tau}$$

where  $\tau \equiv \text{time constant} = RC \text{ or } L/R$

Note: all  $i$ 's and  $v$ 's in the circuit have same time constant.

Now we can write down the formulas given in the answer to the problem.