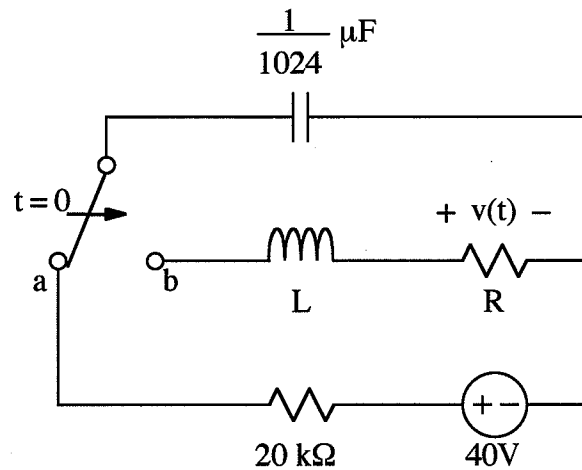


EX:



In the above circuit, the switch moves from a to b at $t = 0$.

Find values of R and L such that the roots of the characteristic equation of the circuit for $t > 0$ are $s_1 = -8 \text{ k rad/s}$ and $s_2 = -512 \text{ k rad/s}$.

Sol'n: After time $t = 0$, the circuit is a series RLC consisting of R , L , and C .

$$\therefore \alpha = \frac{R}{2L}$$

The characteristic roots are

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

where

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

The product of characteristic roots is ω_0^2 :

$$s_1 \cdot s_2 = (-\alpha + \sqrt{\alpha^2 - \omega_0^2})(-\alpha - \sqrt{\alpha^2 - \omega_0^2})$$

$$s_1 \cdot s_2 = (-\alpha)^2 - \sqrt{\alpha^2 - \omega_0^2}^2$$

$$= \alpha^2 - (\alpha^2 - \omega_0^2)$$

$$s_1 \cdot s_2 = \omega_0^2$$

Using $\omega_0^2 = \frac{1}{LC}$, we have

$$L = \frac{1}{C s_1 s_2} = \frac{1}{\frac{1}{1024} \mu\text{F} \cdot 8\text{k} \cdot 512\text{k}}$$

$$= \frac{1024}{4096} \text{ H}$$

$$L = 250 \text{ mH}$$

Now that the L value is known, we find R by relating the characteristic roots to α :

$$\frac{s_1 + s_2}{2} = \frac{-\alpha + \sqrt{\alpha^2 - \omega_0^2} - (\alpha - \sqrt{\alpha^2 - \omega_0^2})}{2}$$

$$\frac{s_1 + s_2}{2} = -\alpha$$

Using $\alpha = R/2L$, we have

$$R = \alpha \cdot 2L = -(s_1 + s_2) L = -(8\text{k} + 512\text{k}) 250 \text{ m}\Omega$$

$$R = 130 \text{ k}\Omega$$