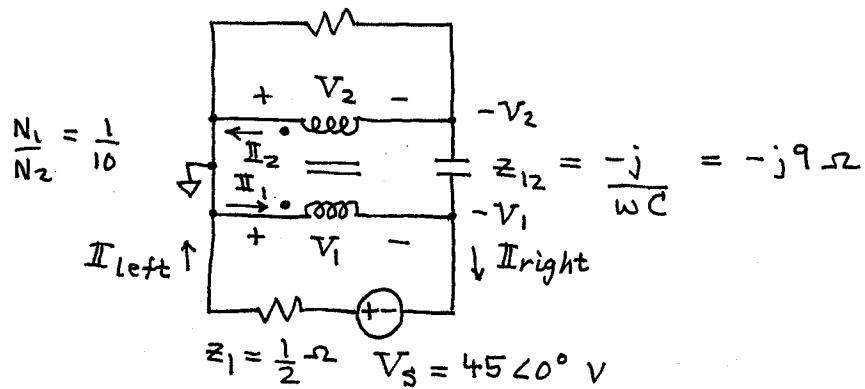


Alternate approach:

$$z_2 = 10 \Omega$$



On the left, we have current

$$I_1 - I_2 + \frac{V_2}{z_2} = I_{\text{left}}$$

On the right, we have current

$$-\frac{V_2 - V_1}{z_{12}} + I_1 = I_{\text{right}}$$

We have  $I_{\text{left}} = I_{\text{right}}$

and the following ideal transformer eqns:

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \equiv N \quad \text{or} \quad V_2 = \frac{V_1}{N}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1} = \frac{1}{N} \quad \text{or} \quad I_2 = I_1 N$$

Making all these substitutions, we have

$$\mathbb{I}_1 - \mathbb{I}_1 N + \frac{V_1}{N} \frac{1}{z_2} = -\frac{V_1}{N} + V_1 + \mathbb{I}_1$$

$\frac{1}{z_{12}}$

or

$$-\mathbb{I}_1 N = V_1 \left[ \frac{\left(1 - \frac{1}{N}\right)}{z_{12}} - \frac{\frac{1}{N}}{\frac{1}{z_2}} \right]$$

or

$$\frac{V_1}{\mathbb{I}_1} = \frac{-N}{\left(1 - \frac{1}{N}\right) \frac{1}{z_{12}} - \frac{1}{N} \frac{1}{z_2}}$$

$$\frac{V_1}{\mathbb{I}_1} = \frac{1}{\frac{1-N}{N^2} \frac{1}{z_{12}} + \frac{1}{N^2} \frac{1}{z_2}}$$

$$\frac{V_1}{\mathbb{I}_1} = z_{12} \frac{N^2}{1-N} \parallel z_2 N^2$$

$$\frac{V_1}{\mathbb{I}_1} = N^2 \cdot \frac{z_{12}}{1-N} \parallel z_2$$

Using the values for this problem:

$$\frac{V_1}{\mathbb{I}_1} = \left(\frac{1}{10}\right)^2 \cdot \frac{-j9}{1 - \frac{1}{10}} \parallel 10 = \left(\frac{1}{10}\right)^2 \cdot \frac{-j9}{\frac{9}{10}} \parallel 10$$

$$" = \left(\frac{1}{10}\right)^2 \cdot -j10 \parallel 10 = \frac{1}{10} \cdot -j \parallel 1 = \frac{1}{10} \frac{-j}{1-j}$$

$$" = \frac{1}{10} \frac{1+j}{1+j} \cdot \frac{-j}{1-j} = \frac{1-j}{20} \parallel 1-j$$

$$\text{or } V_1 = N^2 \cdot \frac{z_{12}}{1-N} \parallel z_2 \cdot I_1 = \frac{1-j_N \cdot I_1}{20}$$

$$\text{We have } I_{\text{left}} = I_1(1-N) + N^2 \frac{z_{12}}{1-N} \parallel z_2 I_1$$

$$N z_2$$

In terms of  $V_1$ , we have

$$I_1 = \frac{V_1}{N^2 \cdot \frac{z_{12}}{1-N} \parallel z_2}$$

$$I_{\text{left}} = \frac{V_1}{N^2 \cdot \frac{z_{12}}{1-N} \parallel z_2} (1-N) + V_1 \frac{1}{N z_2}$$


$$= V_1 \left[ \frac{1-N}{N^2} \left( \frac{1-N}{z_{12}} + \frac{1}{z_2} \right) + \frac{1}{N z_2} \right]$$

$$= V_1 \left[ \frac{(1-N)^2}{N^2} \frac{1}{z_{12}} + \frac{1-N}{N^2} \frac{1}{z_2} + \frac{N}{N^2} \frac{1}{z_2} \right]$$

$$= V_1 \left[ \frac{(1-N)^2}{N^2} \frac{1}{z_{12}} + \frac{1}{N^2 z_2} \right]$$

$$I_{\text{left}} = \frac{V_1}{N^2 \cdot \frac{z_{12}}{(1-N)^2} \parallel z_2}$$
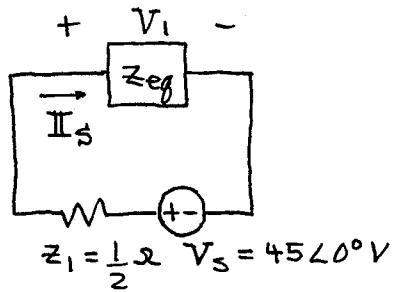
$$\text{We define } z_{eq} = \frac{V_1}{I_{\text{left}}} = N^2 \cdot \frac{z_{12}}{(1-N)^2} \parallel z_2$$



$$V_1 = V_s \cdot \frac{z_{eq}}{z_1 + z_{eq}}$$

$$z_{eq} = N^2 \frac{z_2}{(1-N)^2} \parallel z_2 = \left(\frac{1}{10}\right) \cdot \frac{-j9}{\left(\frac{1}{10}\right)^2} \parallel 10 \Omega$$

$$= \frac{1}{100} \cdot \frac{-j9}{\left(\frac{9}{10}\right)^2} \parallel 10 \Omega$$

$$= \frac{1}{100} \cdot -j \frac{100}{9} \parallel 10 \Omega$$

$$= -j \frac{1}{9} \parallel \frac{1}{10} \Omega$$

$$z_{eq} = \frac{-j}{\frac{90}{10-j\frac{1}{9}}} = \frac{-j}{9-j10} = \frac{1}{10+j9}$$

$$V_1 = V_s \frac{\frac{1}{10+j9}}{\frac{1}{2} + \frac{1}{10+j9}} = 45 \frac{\frac{1}{10+j9}}{\frac{10+j9+1}{2}} V$$

$$V_1 = \frac{45 (z)}{12+j9} V = \frac{90}{12+j9} = \frac{30}{4+j3}$$

$$V_2 = \frac{V_1}{N} = V_1 \cdot 10 = \frac{30 \cdot 10}{4+j3}$$

$$I = -\frac{V_2}{Z_2} = -\frac{30 \cdot 10}{4+j3} \cdot \frac{1}{j0} = -\frac{30}{4+j3}$$

$$= -\frac{30}{25} (4-j3) A$$

$$= -\frac{6}{5} (4-j3) = -\frac{6}{5} \cdot 5 \angle -36.9^\circ A$$

$$I = 6 \angle 143.1^\circ A$$

$$i(t) = 6 \cos(\omega t + 143.1^\circ) A, \quad \omega = \frac{20 \cdot 10^4}{9} \text{ r/s}$$