
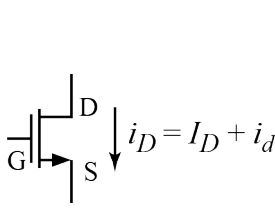


TOOL: AC Model of enhancement-mode NMOS FET with channel modulation.


Transconductance parameter	k_n	A/V ²	$k_n = \sqrt{\mu_n C_{ox} \frac{W}{L}}$
Threshold	V_{TH}	V	
Channel modulation	λ	/V	
Early voltage	V_A	/V	
Channel modulation R	r_o	Ω	$r_o = \frac{1}{\lambda I_D} = \frac{V_A}{I_D}$
Over-voltage	V_{OV}	V	$V_{OV} = V_{GS} - V_{TH}$
DC Drain current	I_D	A	
AC drain current	i_d	A	
AC transconductance	g_m	A/V	

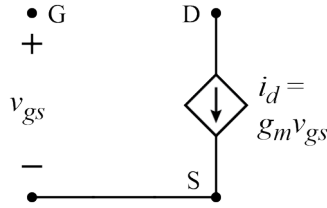

FET



AC model

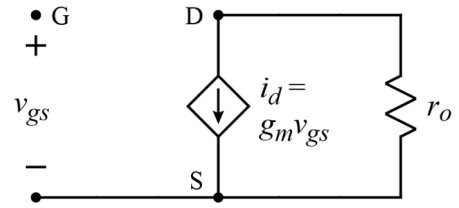

AC model with channel modulation

MODEL: Without channel modulation: $I_D = \frac{k_n}{2}(V_{GS} - V_{TH})^2$

$$i_d = g_m v_{gs}$$

$$g_m = k_n(V_{GS} - V_{TH})$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}}$$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L}} I_D$$

$$r_o = \infty \Omega \text{ (omitted from schematic)}$$

With channel modulation: $I_{Dmod} = \frac{k_n}{2}(V_{GS} - V_{TH})^2(1 + \lambda V_{DS})$

$$i_{dmod} = g_m v_{gs} + v_{ds}/r_o$$

$$g_m = \frac{dI_{Dmod}}{dV_{GS}} \quad g_m = k_n(V_{GS} - V_{TH})(1 + \lambda V_{DS}) \quad g_m = \frac{2I_{Dmod}}{V_{GS} - V_{TH}}$$

$$r_o = \frac{1}{\frac{dI_{Dmod}}{dV_{DS}}} = \frac{1}{\lambda I_{Dmod}} = \frac{V_A}{I_{Dmod}} \text{ where } V_A \text{ is from data sheet}$$

- REF:** [1] Adel S. Sedra and Kenneth C. Smith, *Microelectronic Circuits, 5th Ed.*, New York, NY: Oxford University Press, 2004.
- [2] Behzad Razavi, *Fundamentals of Microelectronics with Robotics and Bioengineering Applications, 3rd Ed., Enhanced eText*, New York, NY: Wiley, 2021. ISBN: 9781119694397
- [3] Becker (<https://electronics.stackexchange.com/users/309451/becker>), Does channel length modulation take effect in triode region of MOSFET?, URL (version: 2024-10-09): <https://electronics.stackexchange.com/q/727466>
- [4] Hearth (<https://electronics.stackexchange.com/users/57556/hearth>), Does channel length modulation take effect in triode region of MOSFET?, URL (version: 2024-10-09): <https://electronics.stackexchange.com/q/727468>